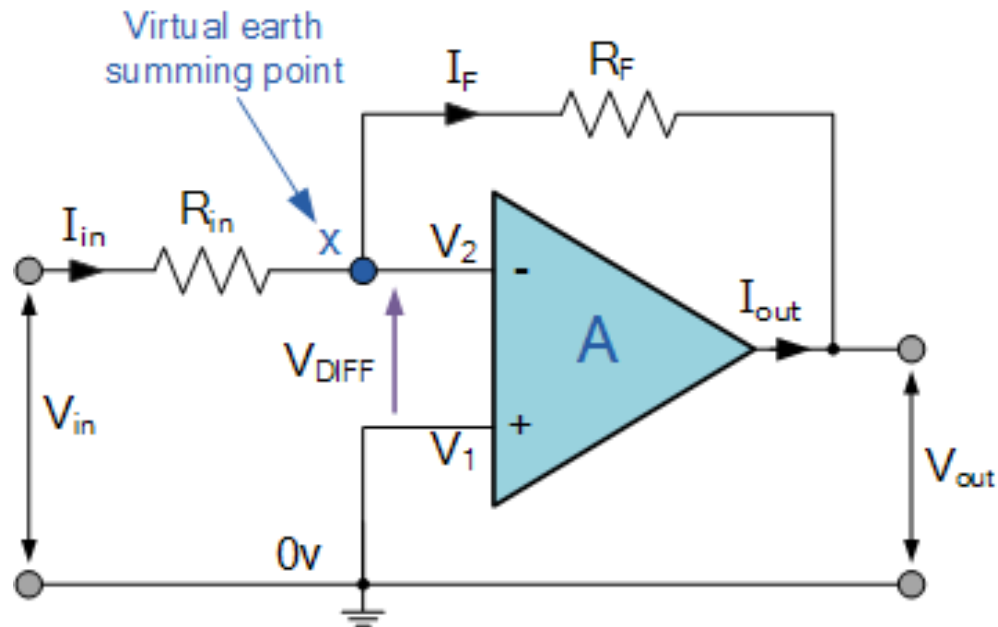


Circuits for Sensors




Inverting Operational Amplifier




$$A_v = \frac{V_{out}}{V_{in}} = -\frac{R_f}{R_{in}}$$

Non-inverting Operational Amplifier

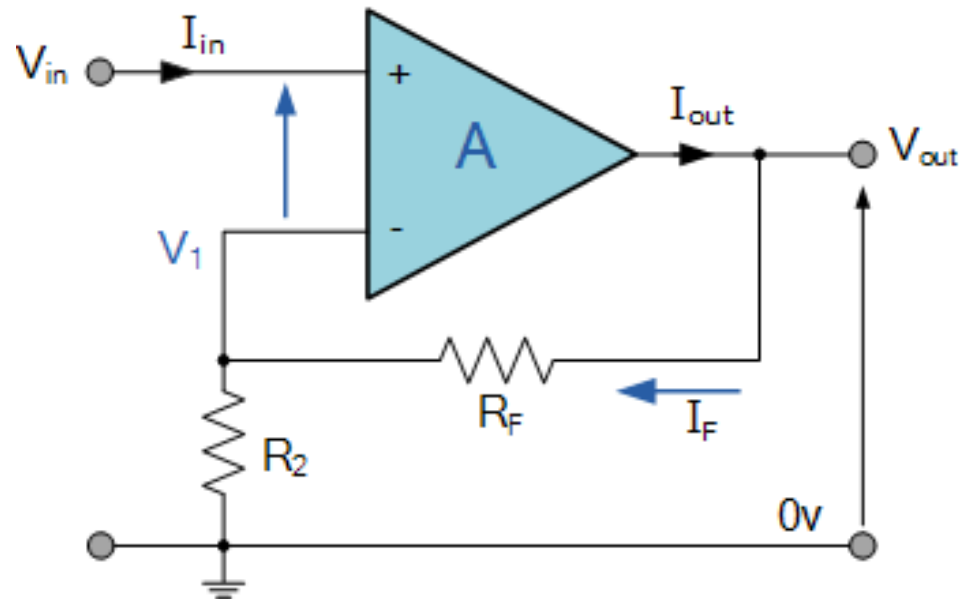


$$A_v = 1 + \frac{R_F}{R_2}$$

Voltage follower (pre-amplifier)

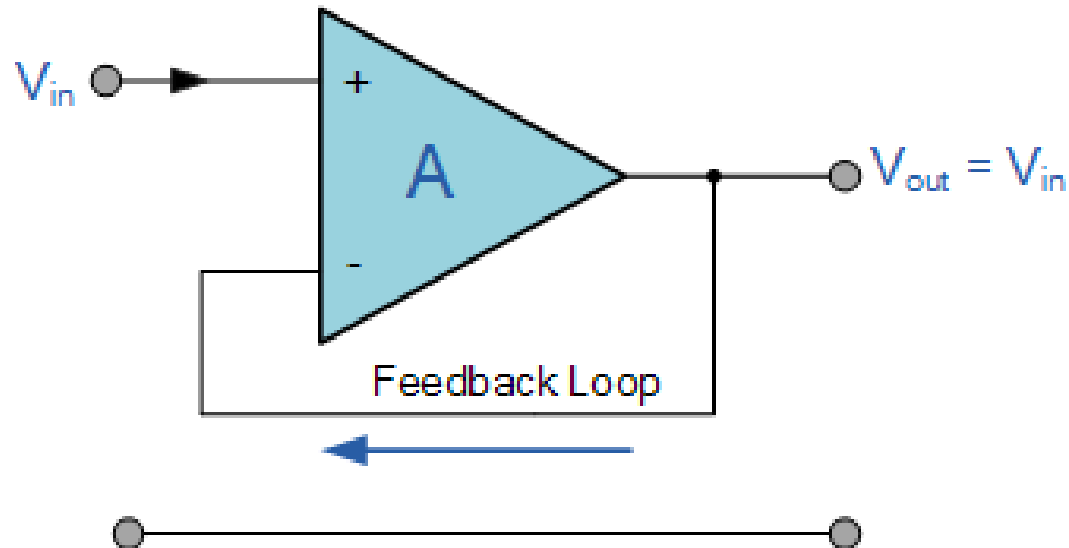

$$A_v = 1$$

Differential Amplifier

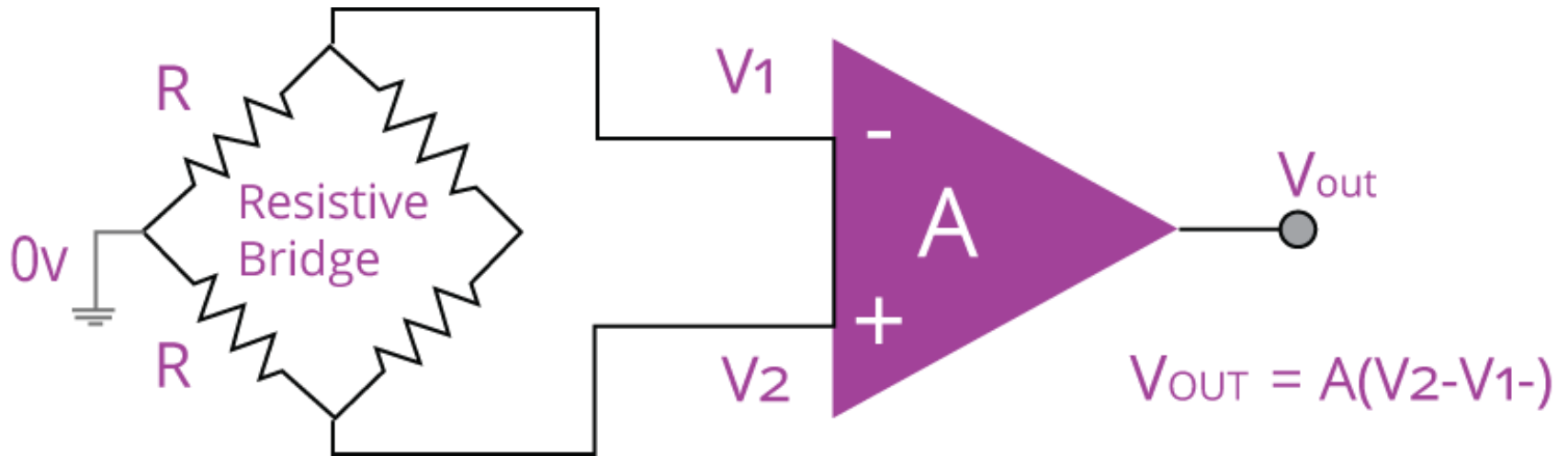


Differential Amplifier

□ Op-Amp as Differential Amplifier


$$v_0 = \frac{R_4}{R_3 + R_4} \left(\frac{R_1 + R_2}{R_1} \right) v_{i2} - \frac{R_2}{R_1} v_{i1}$$

If $R_1 = R_3$ and $R_2 = R_4$

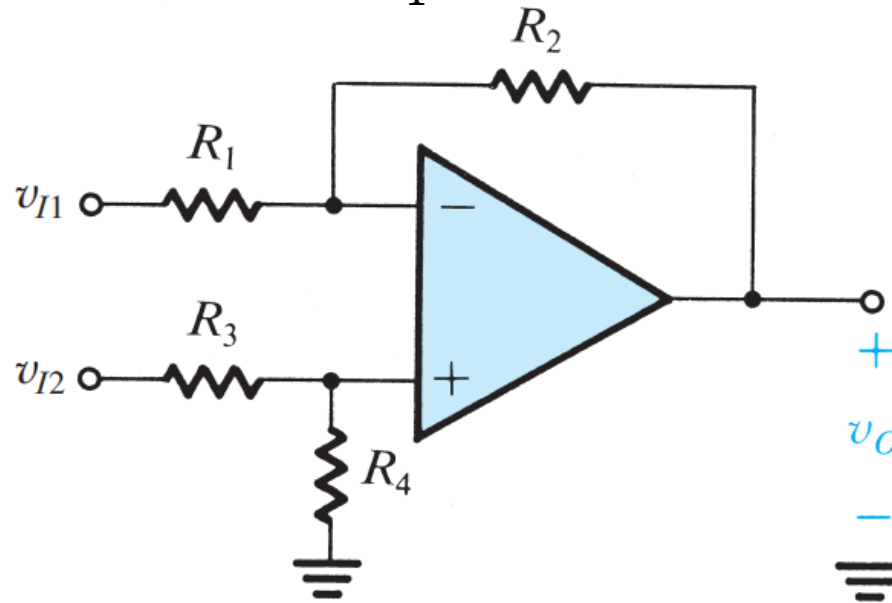
$$v_0 = \frac{R_2}{R_1} (v_{i2} - v_{i1})$$



Differential Amplifier

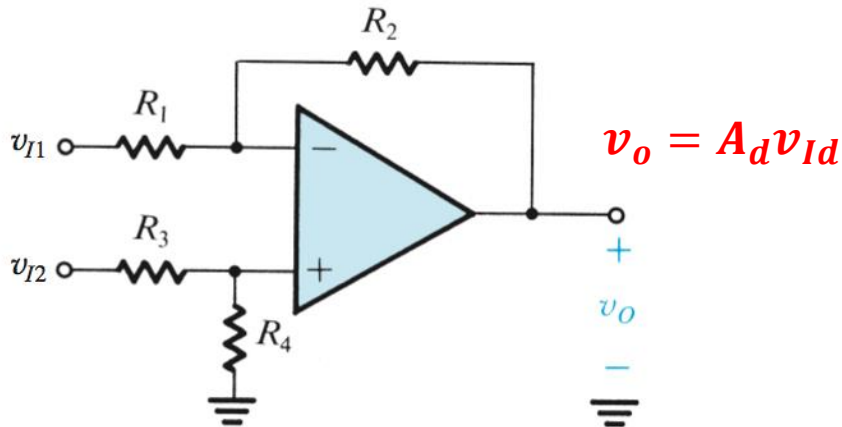

Differential gain

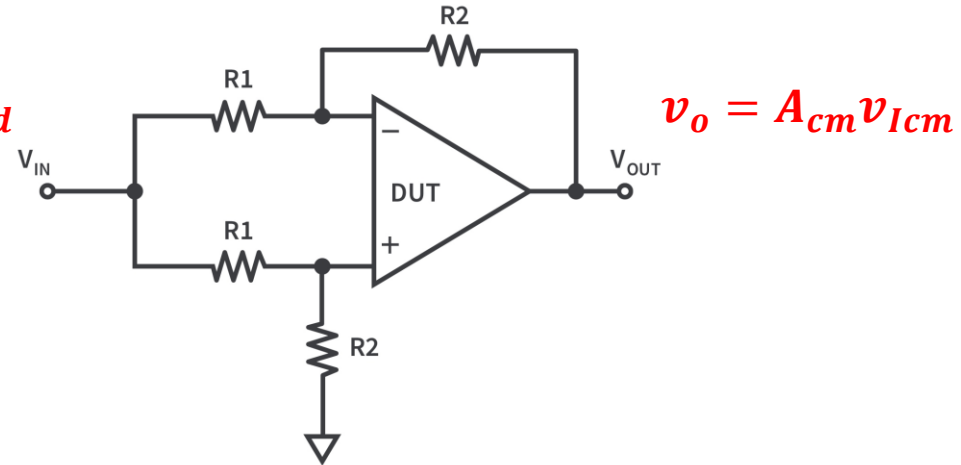



Common-mode gain

$$v_o = A_d v_{Id} + A_{cm} v_{Icm}$$


Common-Mode Rejection Ratio (CMRR)

$$CMRR = 20 \log \frac{A_d}{A_{cm}}$$

Differential Amplifier

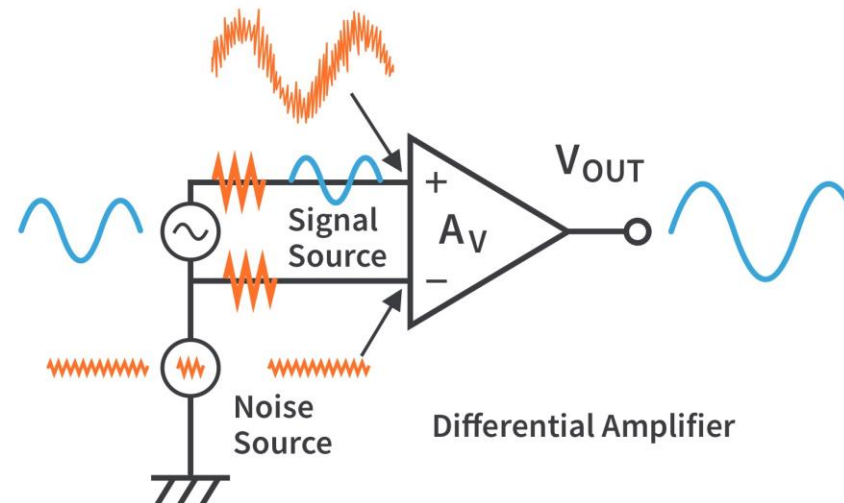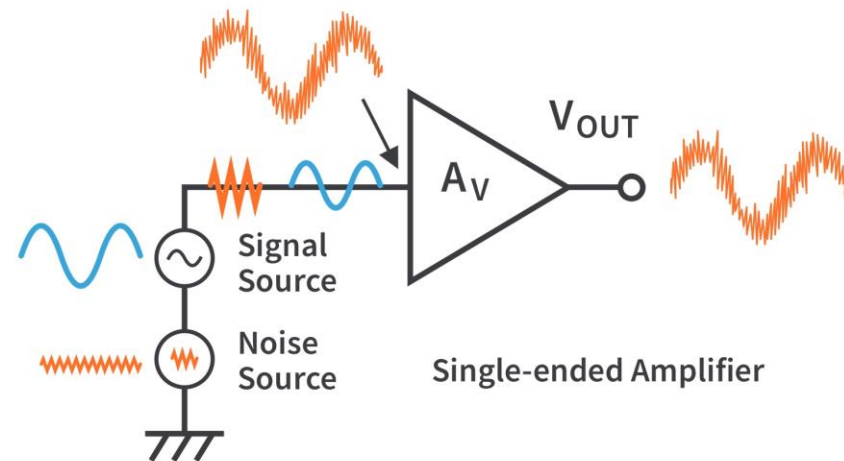

Differential Amplifier

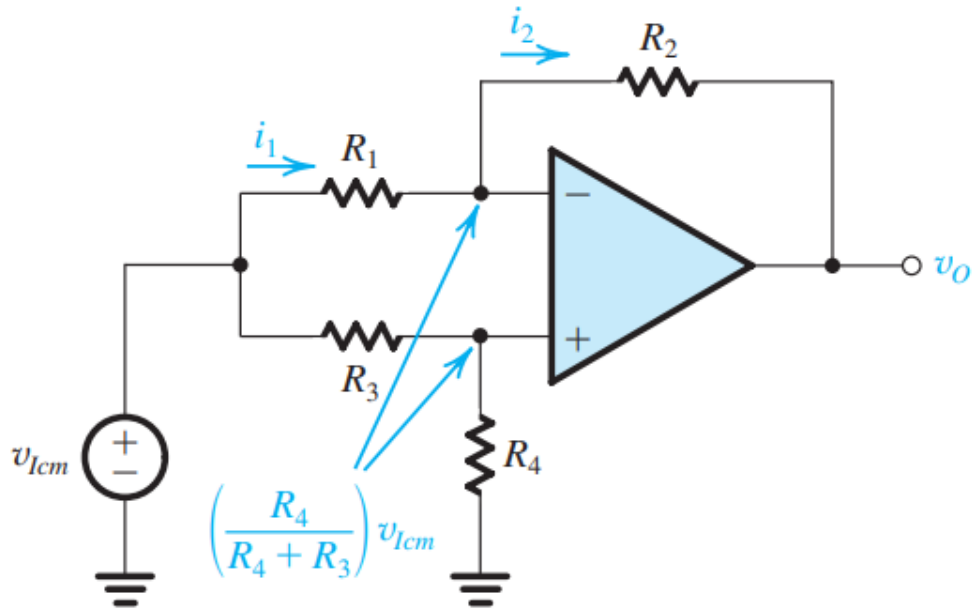

$$v_o = \frac{R_4}{R_4 + R_3} \left(1 - \frac{R_2 R_3}{R_1 R_4} \right) v_{Icm}$$

Common mode gain


$$A_{cm} = \frac{v_o}{v_{Icm}} = \left(\frac{R_4}{R_4 + R_3} \right) \left(1 - \frac{R_2 R_3}{R_1 R_4} \right)$$

Ideally, $R_1 = R_3$ and $R_2 = R_4$

$$A_{cm} = 0 \text{ and } CMRR = \infty$$

Any mismatch in the resistance ratios can make A_{cm} nonzero

Differential Amplifier

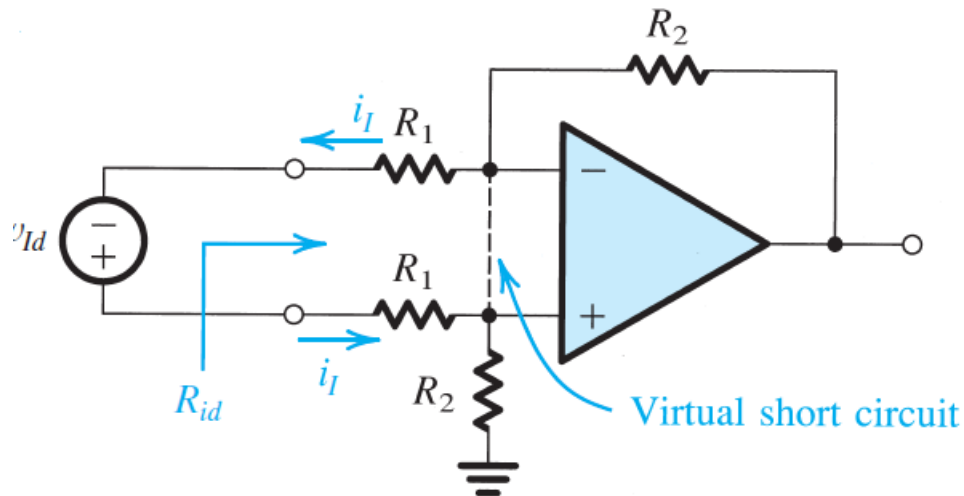



□ Differential input resistance

$$R_{id} \equiv \frac{v_{Id}}{i_I}$$


$$v_{Id} = R_1 i_I + R_1 i_I$$

$$R_{id} = 2R_1$$

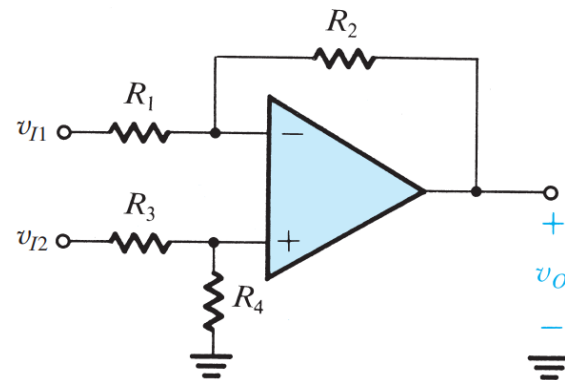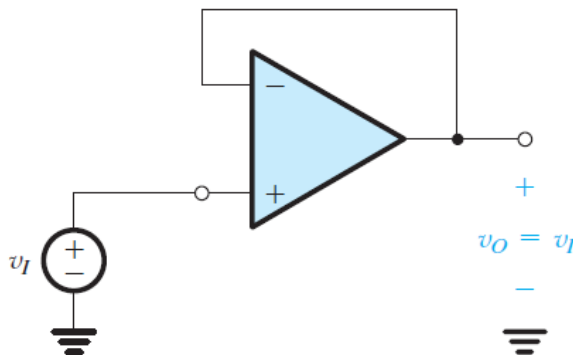
- High input impedance: ✗
- Low output impedance: ✓
- High gain: ✗
- High CMRR: ✗




Instrumentation Amplifier

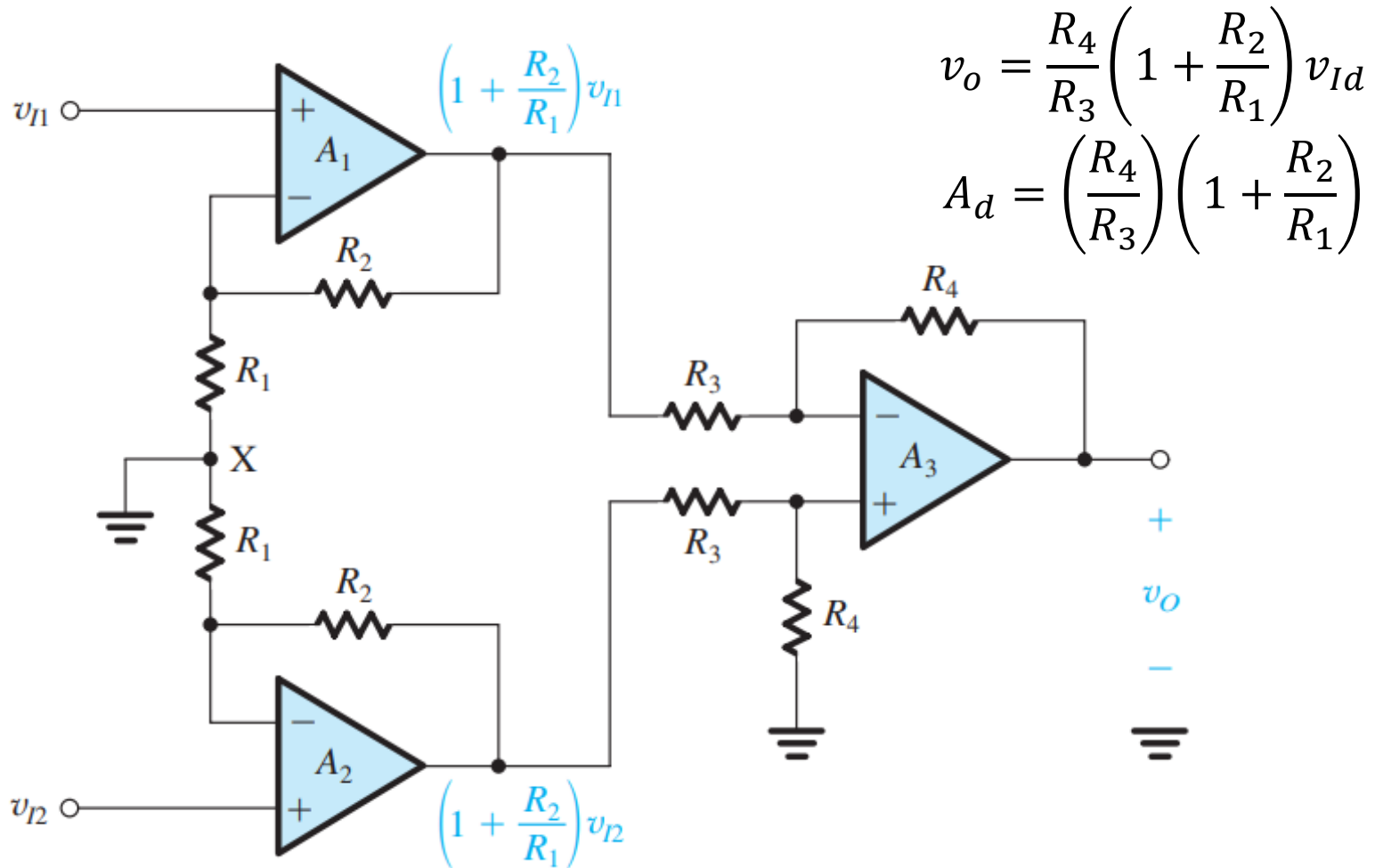


Instrumentation Amplifier

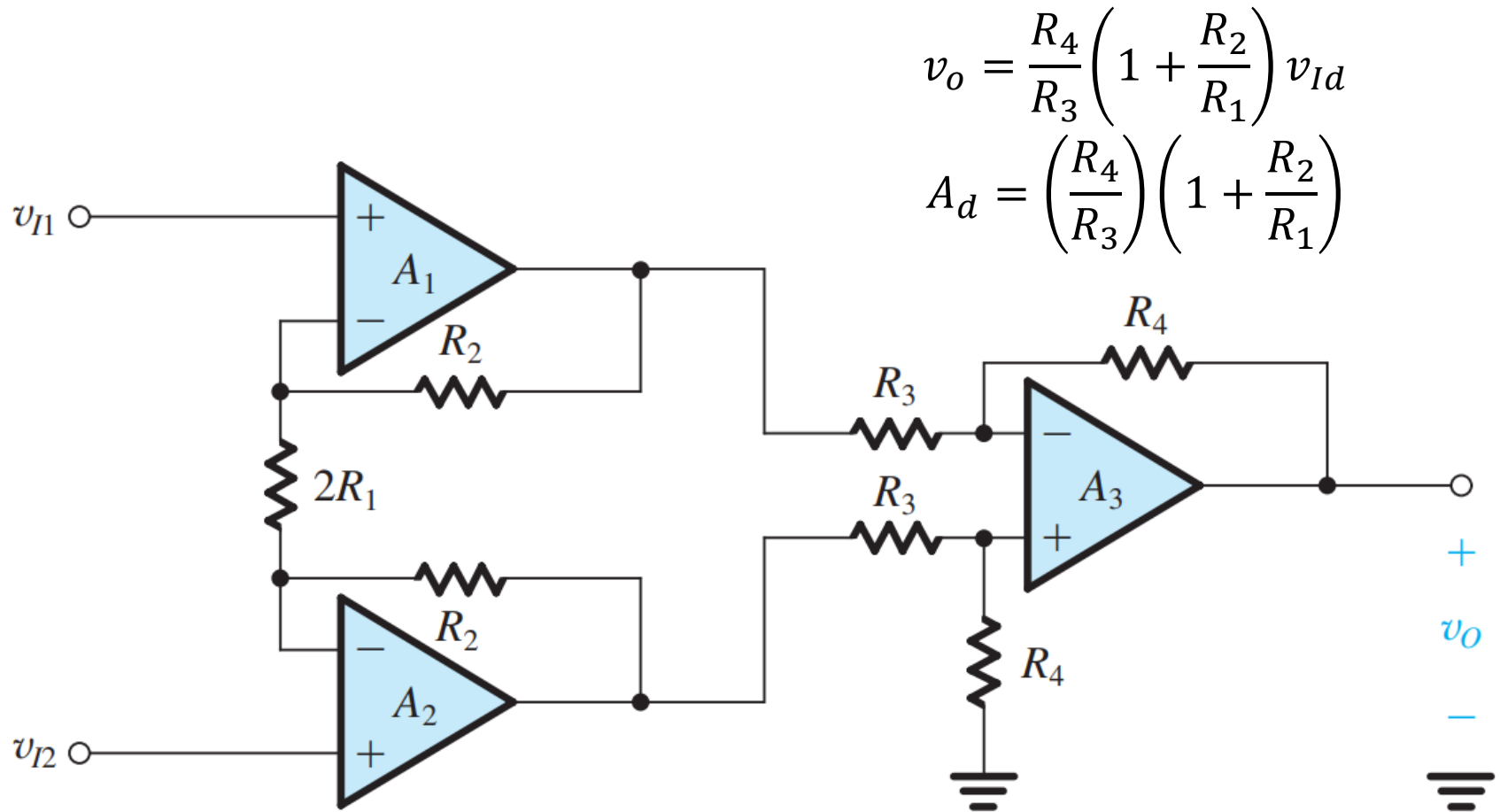

Instrumentation Amplifier

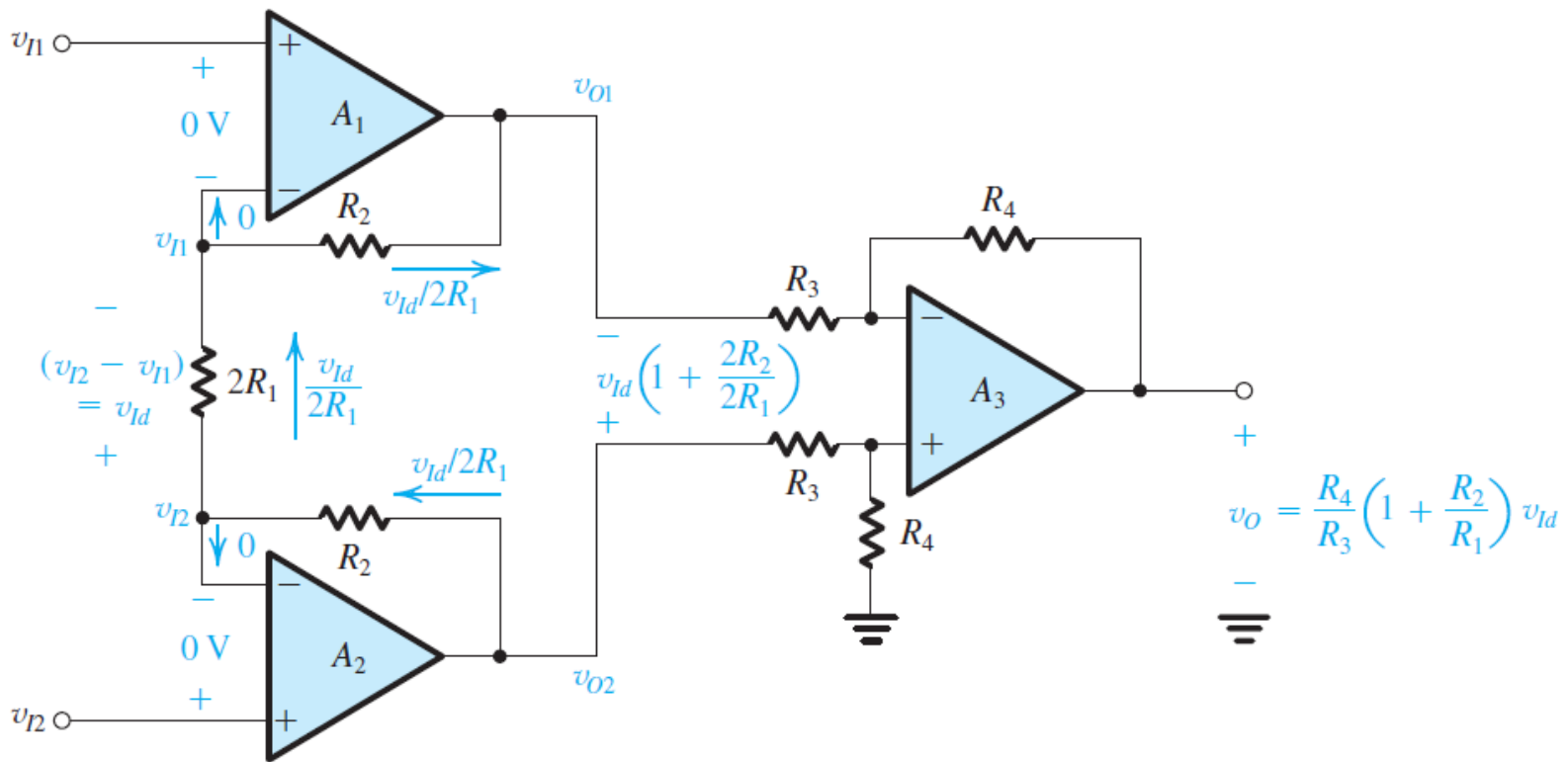


Instrumentation Amplifier

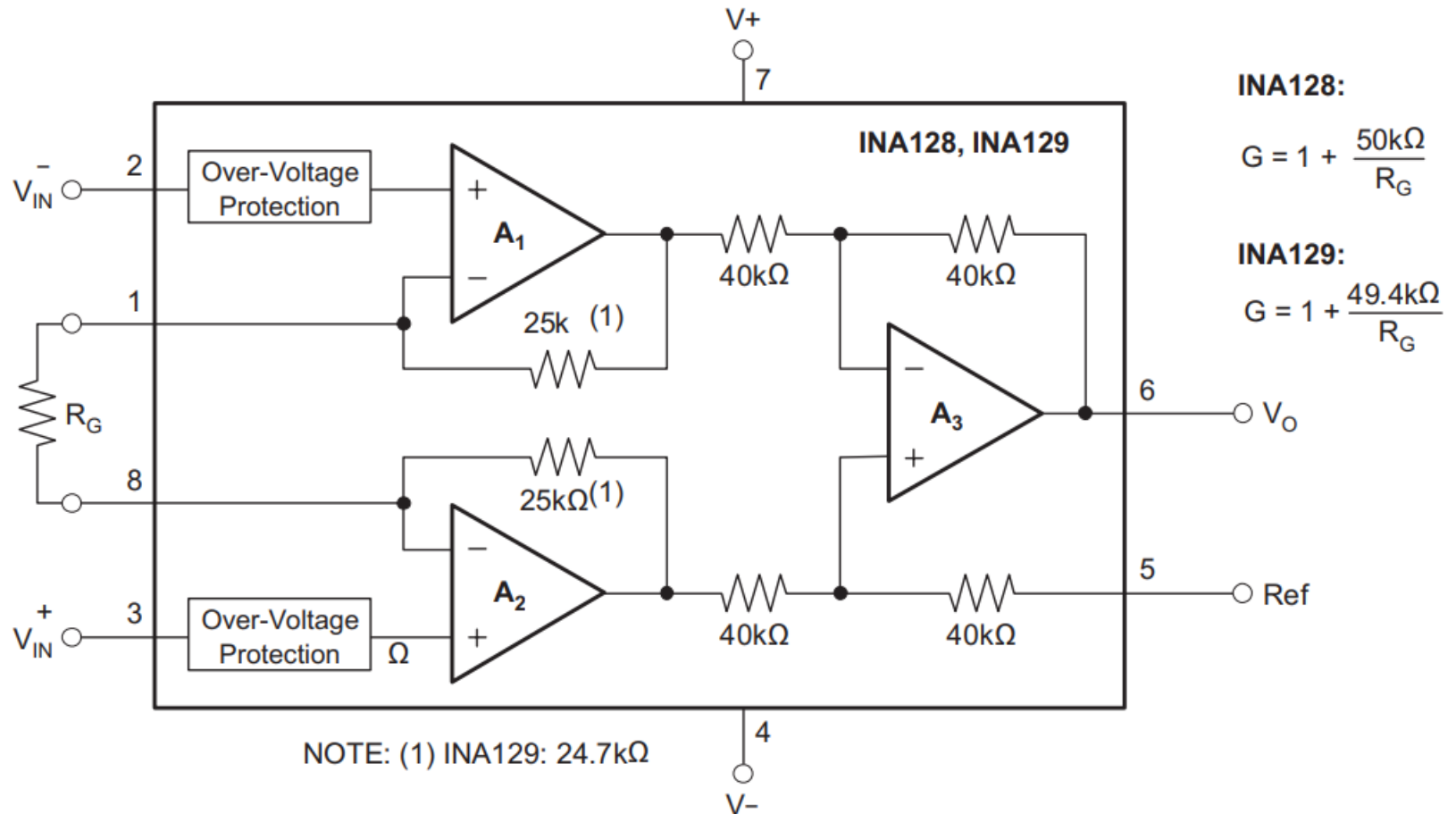


Lock-in amplifier

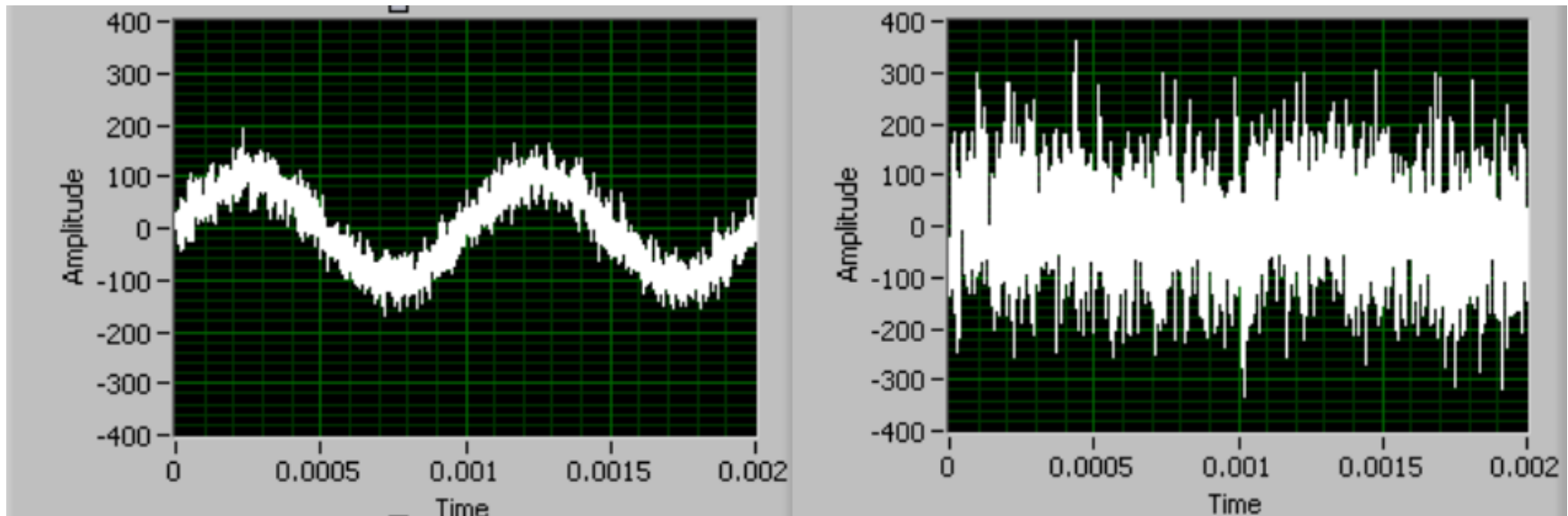
- Detect and measure very small AC signals (down to a few nanovolts) even when the small signal is obscured by larger noise source.



Lock-in Amplifier

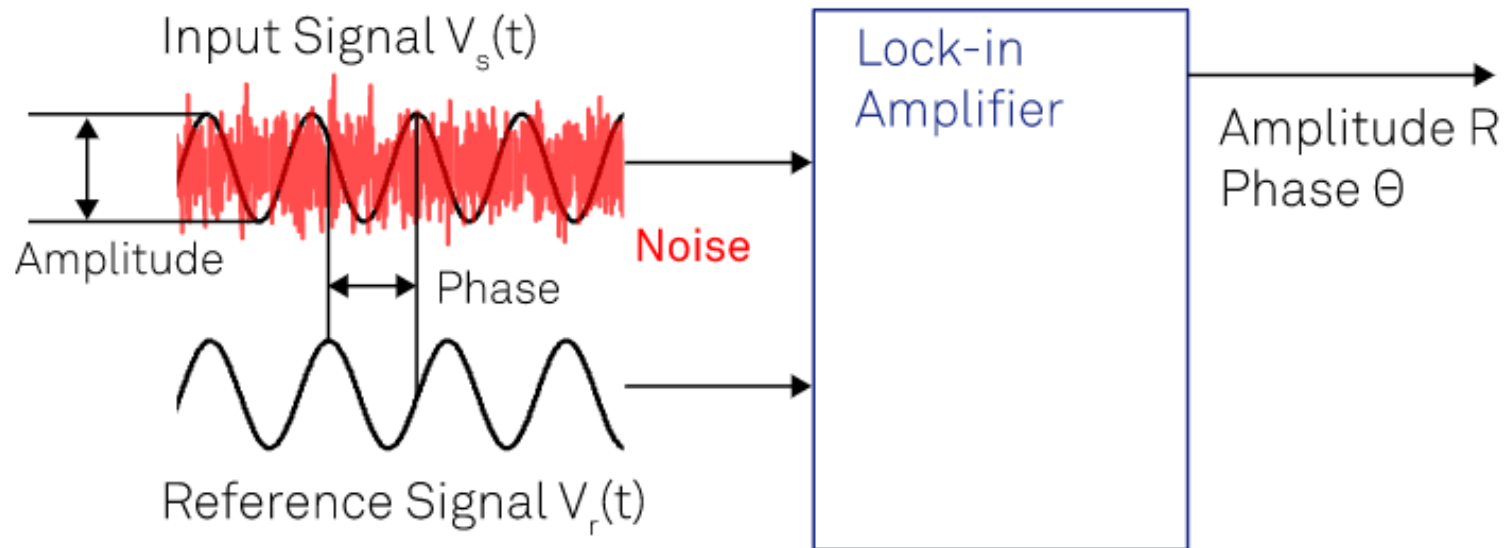

Lock-in amplifier

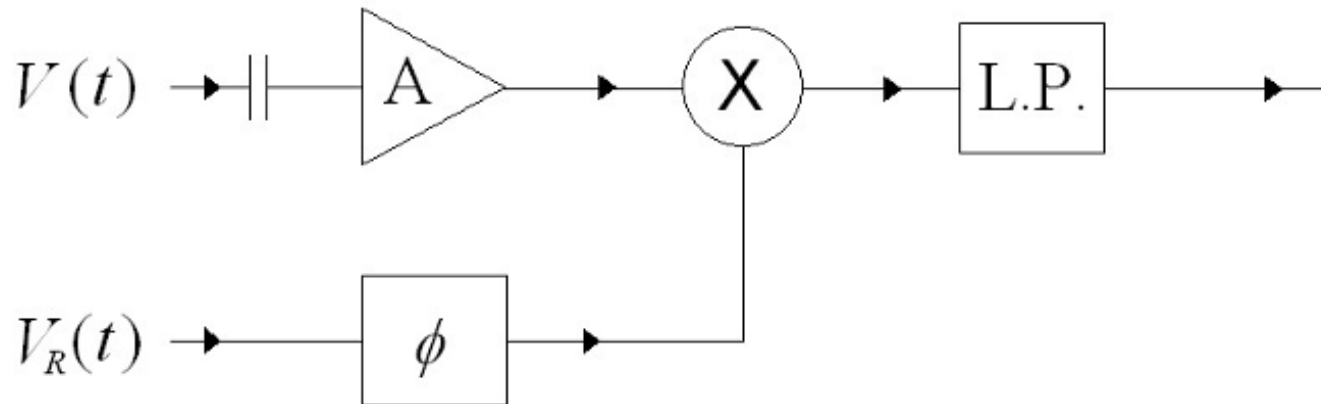


Lock-in amplifier

□ Signal of interest: $V_{sig} \sin(\omega_r t + \theta_{sig})$

□ Reference signal: $V_L \sin(\omega_o t + \theta_{ref})$


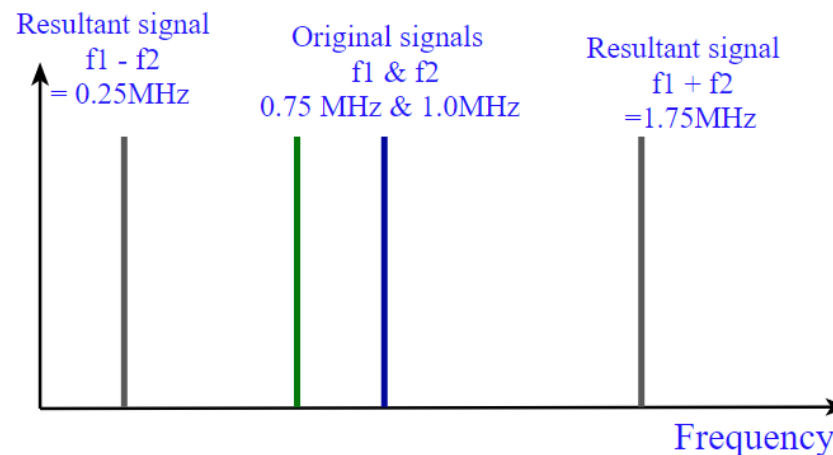
$$\begin{aligned} V_{psd} &= V_{sig} V_L \sin(\omega_r t + \theta_{sig}) \sin(\omega_L t + \theta_{ref}) \\ &= \frac{1}{2} V_{sig} V_L \cos([\omega_r - \omega_L]t + \theta_{sig} - \theta_{ref}) \\ &\quad - \frac{1}{2} V_{sig} V_L \cos([\omega_r + \omega_L]t + \theta_{sig} + \theta_{ref}) \end{aligned}$$



Lock-in amplifier

- If $\omega_L = \omega_r$, the difference frequency component will be a DC signal.

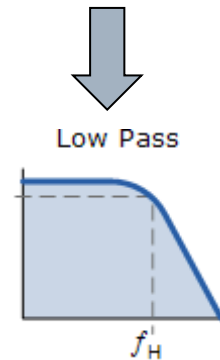
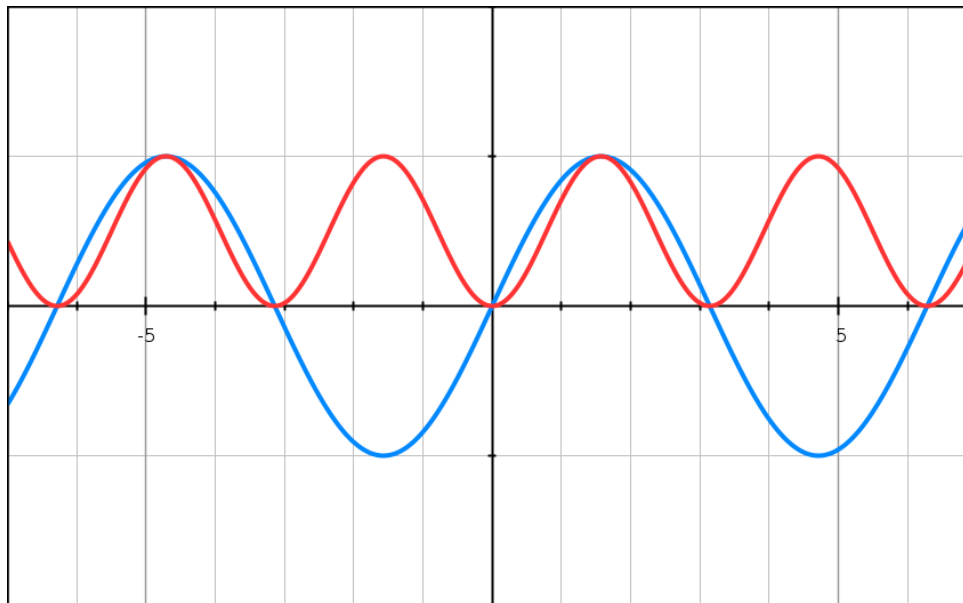
$$V_{psd} = \frac{1}{2} V_{sig} V_L \cos(\theta_{sig} - \theta_{ref}) - \frac{1}{2} V_{sig} V_L \cos(2\omega t + \theta_{sig} + \theta_{ref})$$



Lock-in amplifier



- If $\omega_L = \omega_r$, the difference frequency component will be a DC signal.
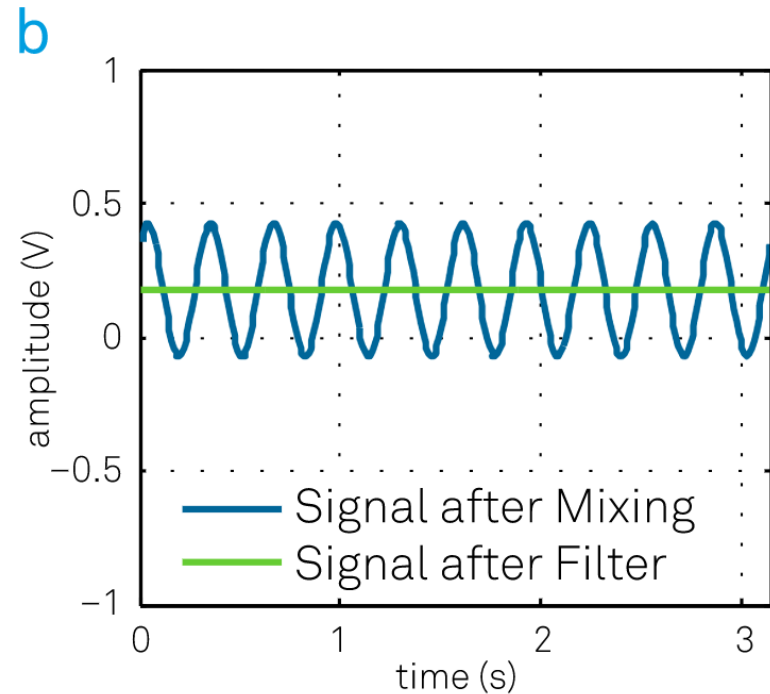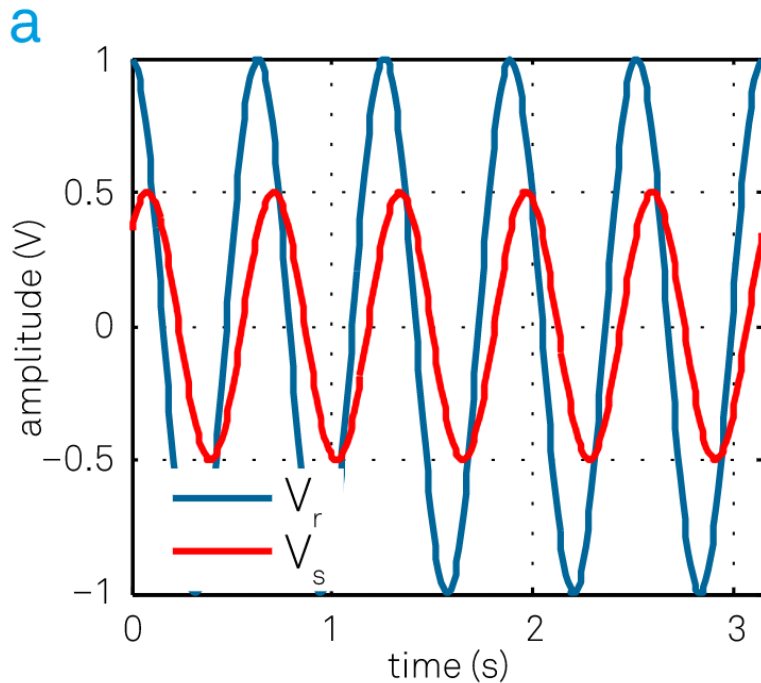
$$V_{psd} = \frac{1}{2} V_{sig} V_L \cos(\theta_{sig} - \theta_{ref}) - \frac{1}{2} V_{sig} V_L \cos(2\omega t + \theta_{sig} + \theta_{ref})$$





Lock-in amplifier

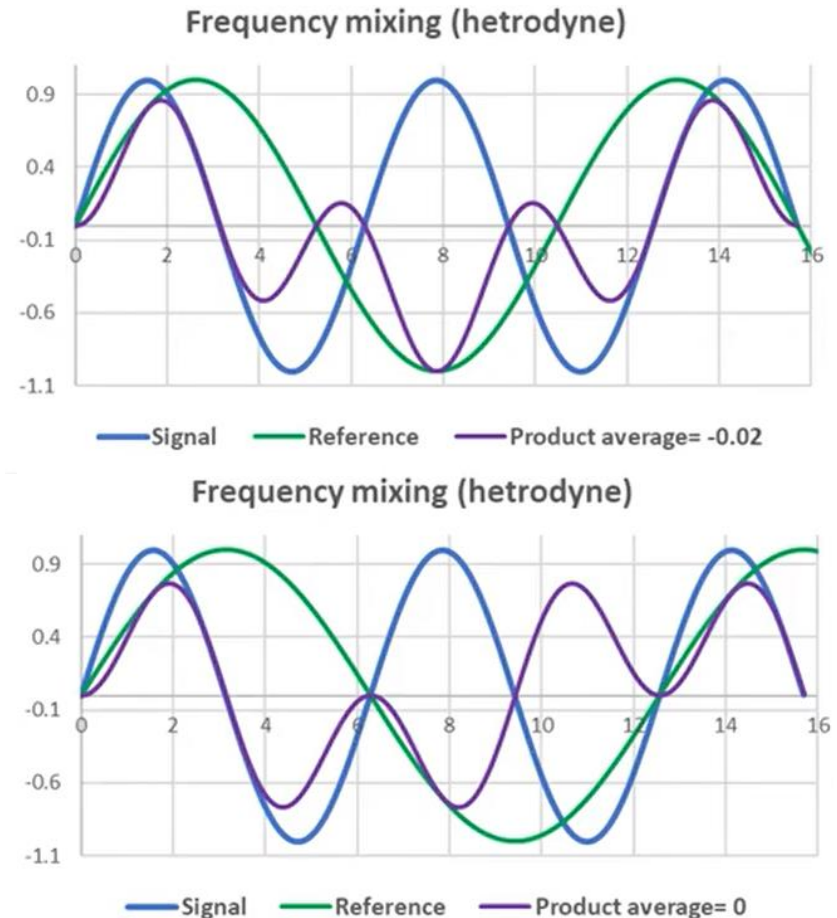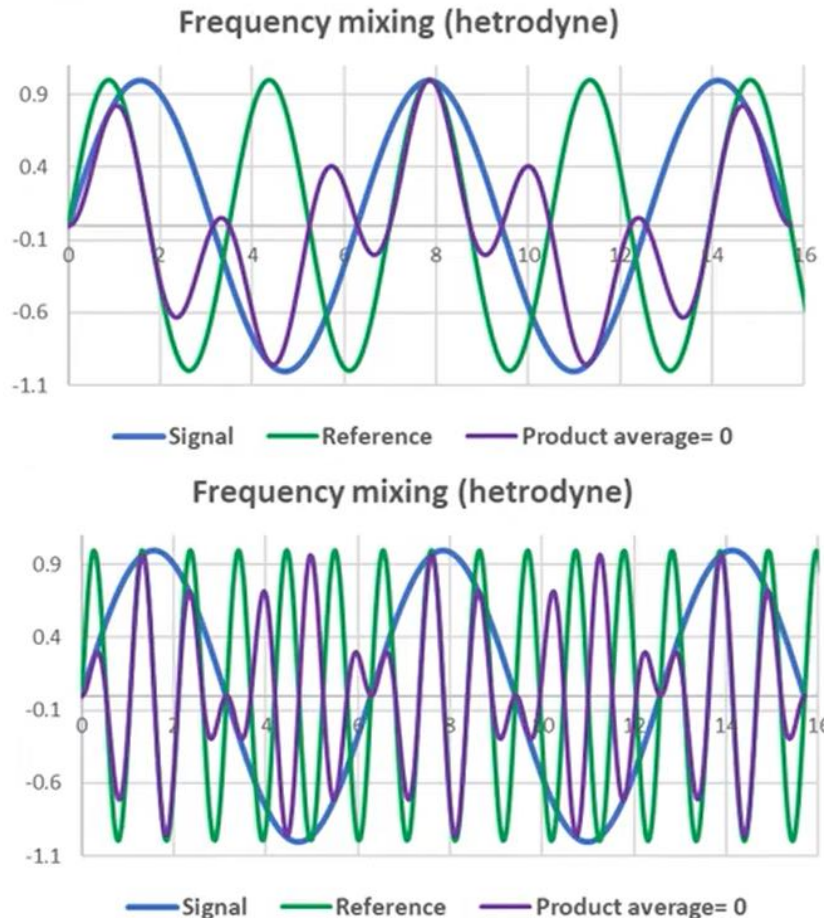- If $\omega_L \neq \omega_r$, signal components with different frequencies make new signals, but they still have **an average value of zero**



Lock-in amplifier

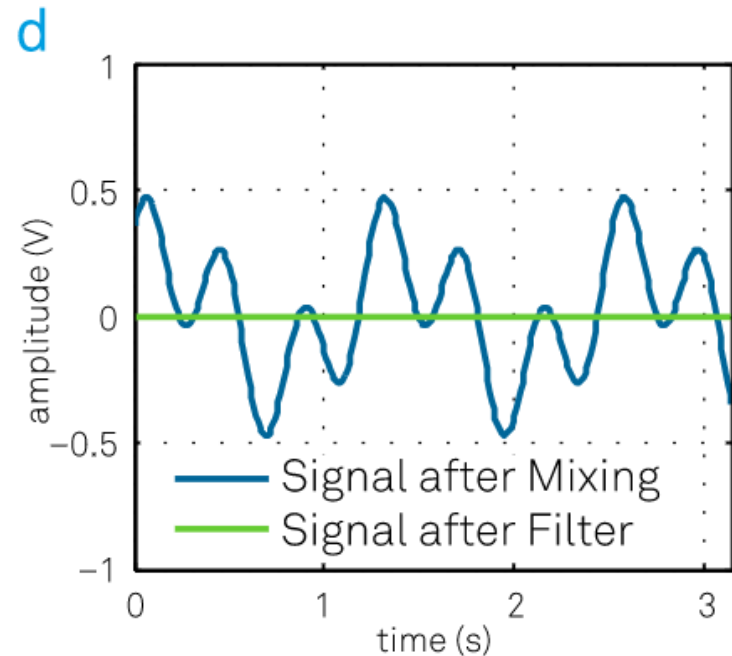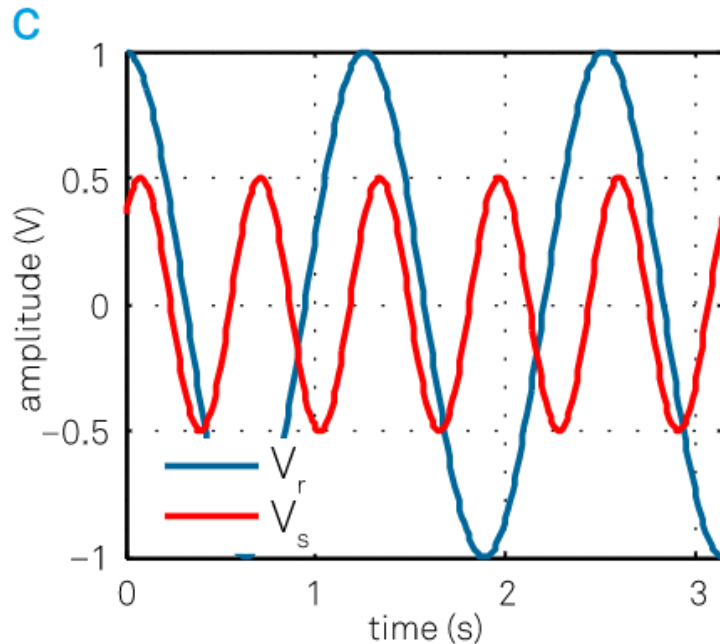
- If $\omega_L \neq \omega_r$, signal components with different frequencies make new signals, but they still have **an average value of zero**



Lock-in amplifier

$$\square \quad X = \frac{1}{2} V_{sig} V_L \cos(\theta_{sig} - \theta_{ref})$$

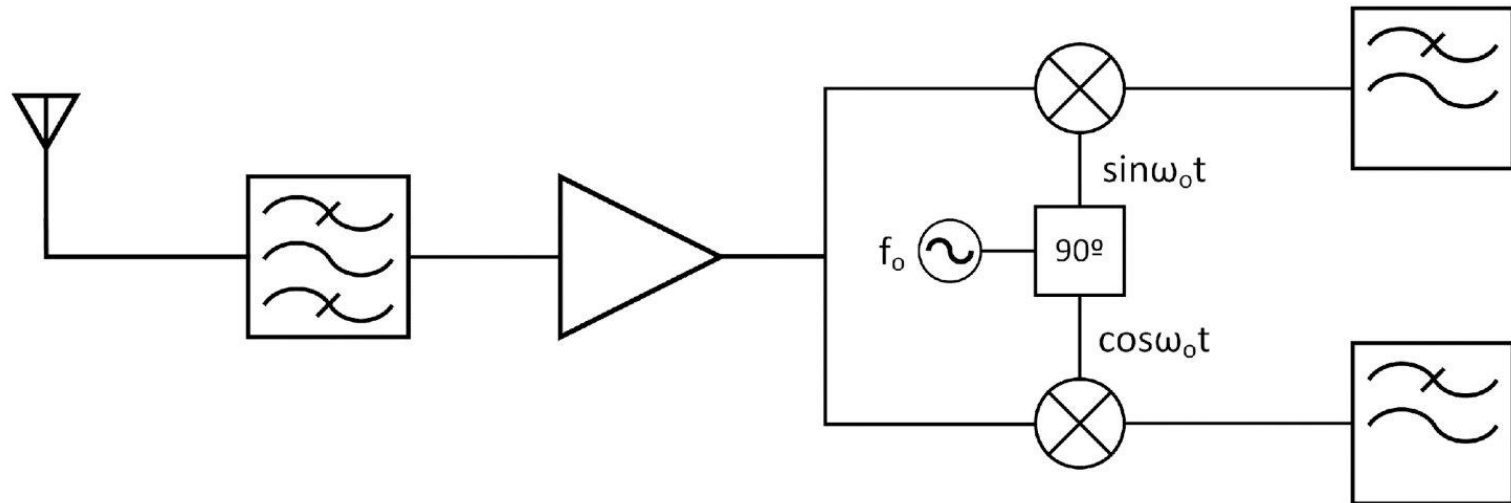
$$\square \quad Y = \frac{1}{2} V_{sig} V_L \sin(\theta_{sig} - \theta_{ref})$$



$$A = 2 \times \sqrt{X^2 + Y^2}$$


$$Phase = \tan^{-1} \frac{Y}{X}$$

Log Amplifier

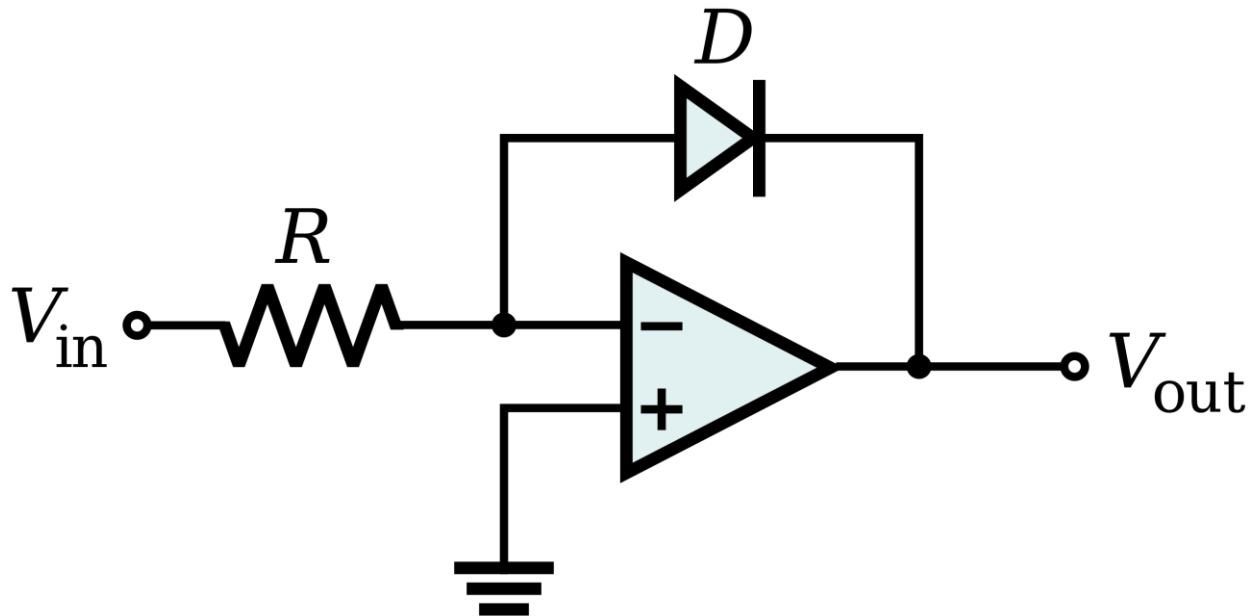


$$V_{out} = -V_T \ln \frac{V_{in}}{I_S R}$$

Anti-Log Amplifier

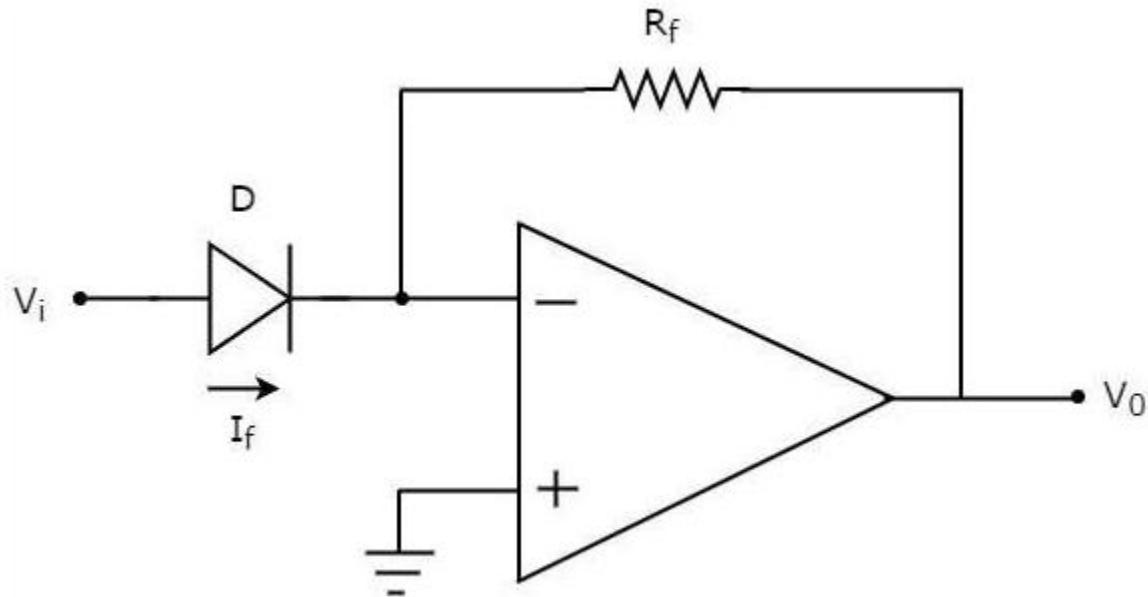


$$V_{out} = -R_f I_s e^{\left(\frac{V_i}{V_T}\right)}$$

Bias (zero drift) removal

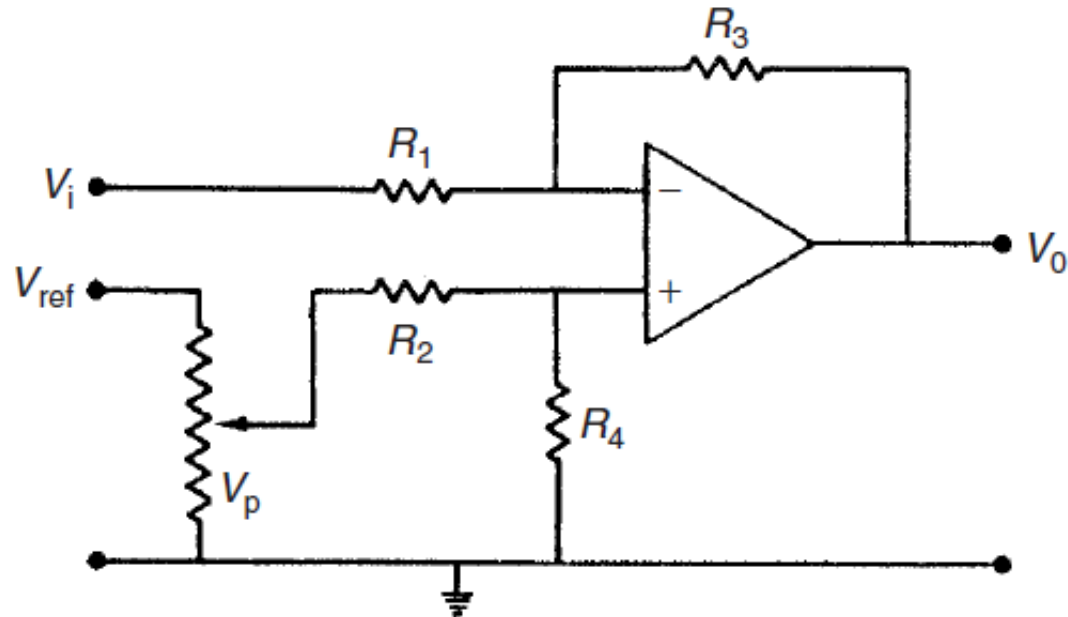


Signal integration

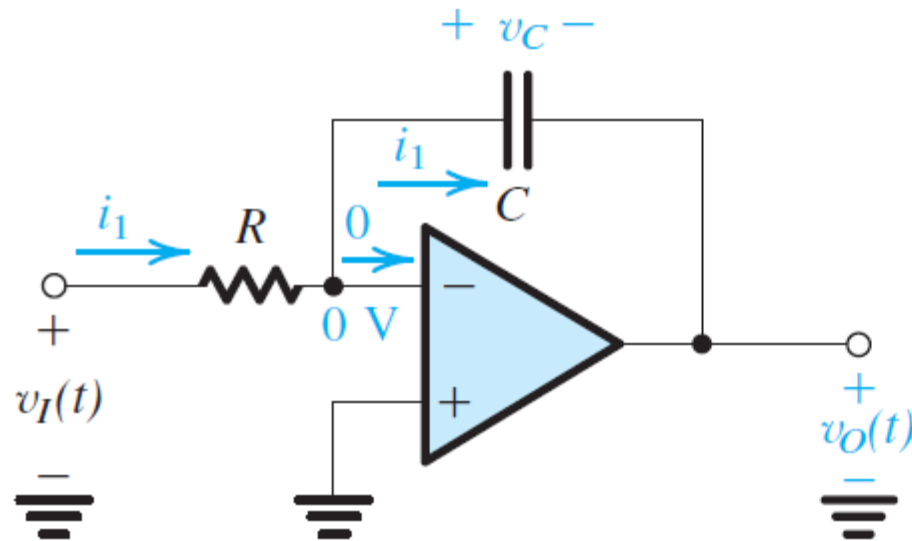

$$v_O(t) = -\frac{1}{CR} \int_0^t v_I(t) dt - V_C$$

$$\frac{V_o}{V_i} = -\frac{1}{sCR}$$



Signal differentiation

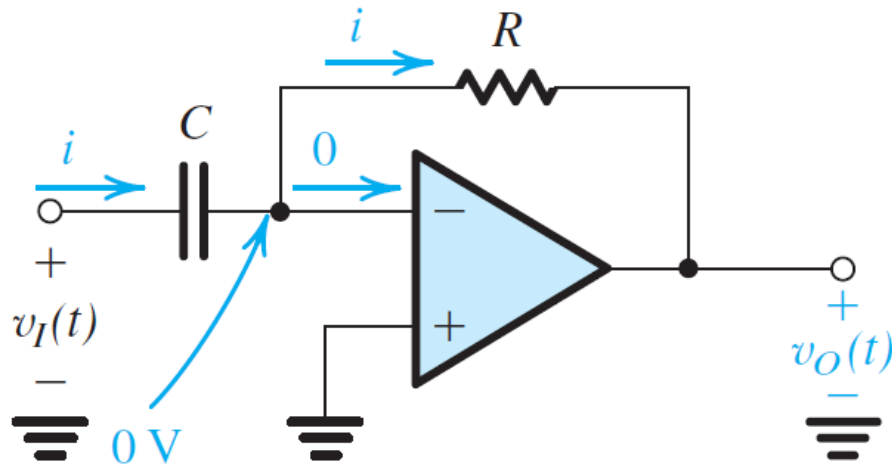




$$i(t) = C \frac{dv_I(t)}{dt}$$
$$v_O(t) = -CR \frac{dv_I(t)}{dt}$$
$$\frac{V_o}{V_i} = -sCR$$

Voltage comparator

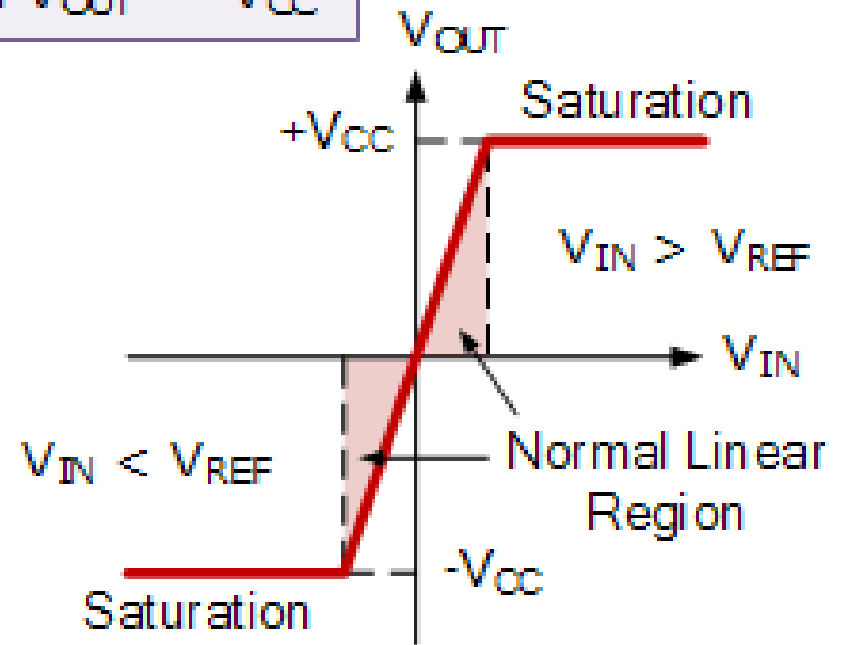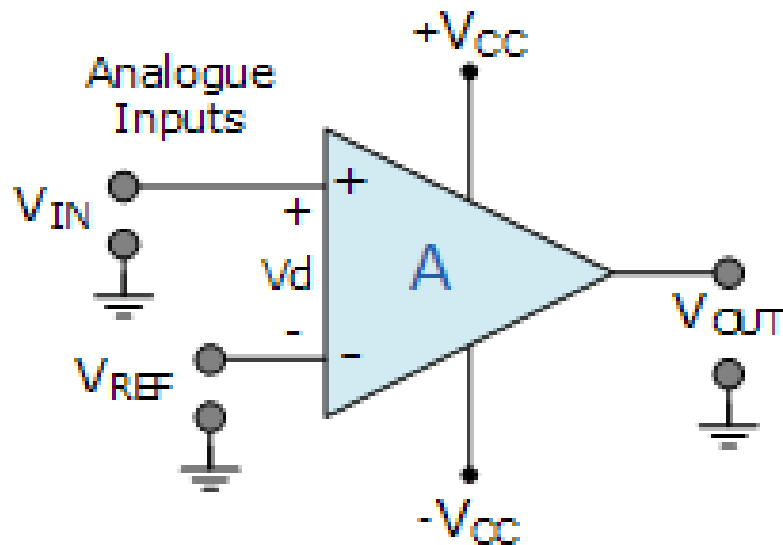
If $V_{IN} > V_{REF}$ then $V_{OUT} = +V_{CC}$
If $V_{IN} < V_{REF}$ then $V_{OUT} = -V_{CC}$



Schmitt trigger

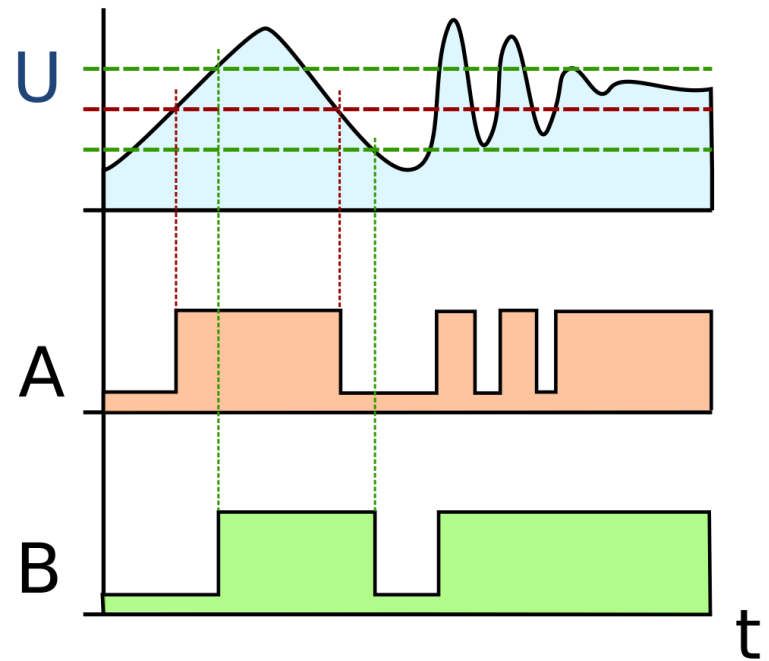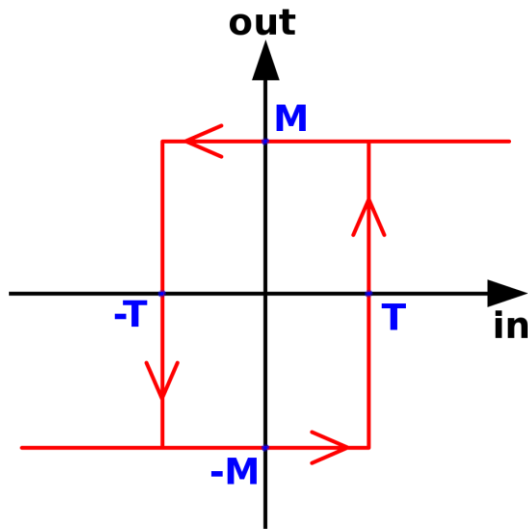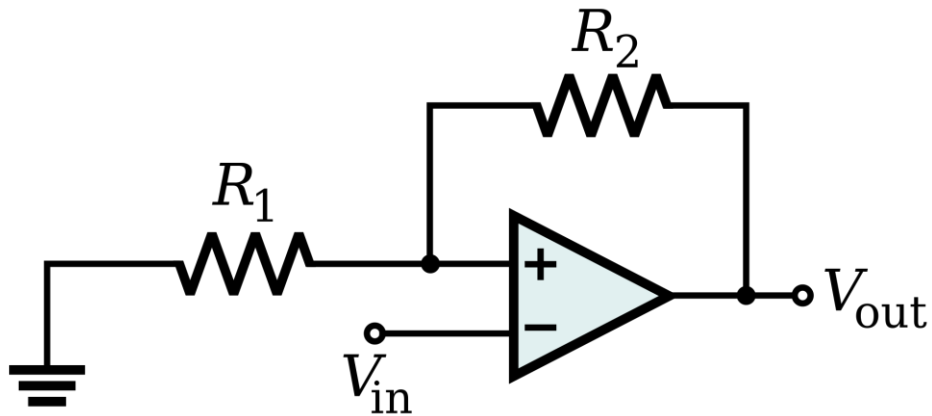


Signal addition



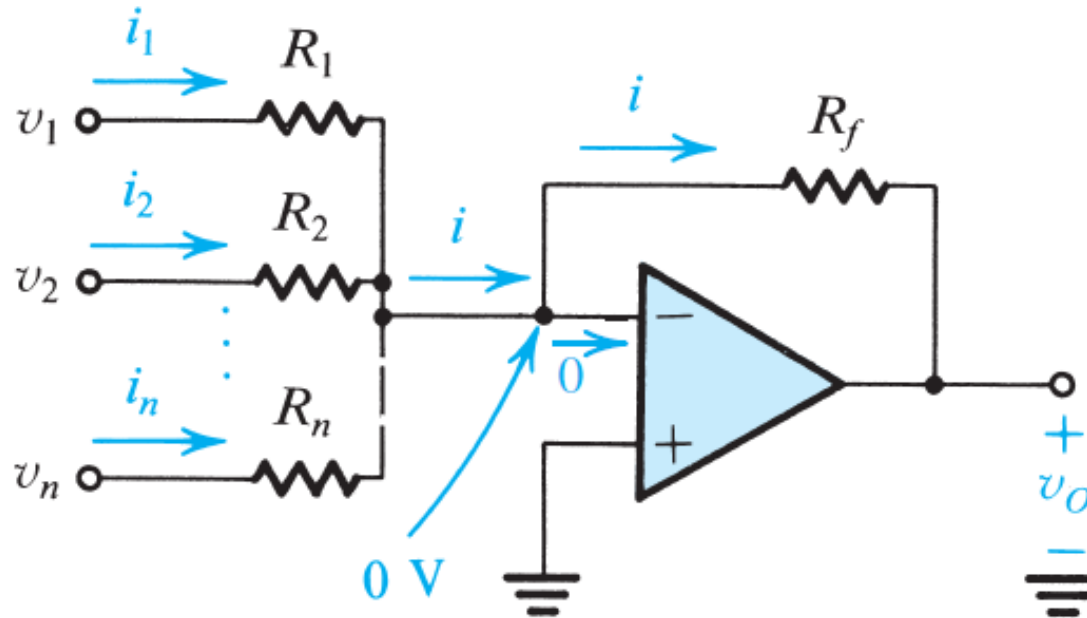


$$v_O = - \left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \dots + \frac{R_f}{R_n} v_n \right)$$


Signal multiplication

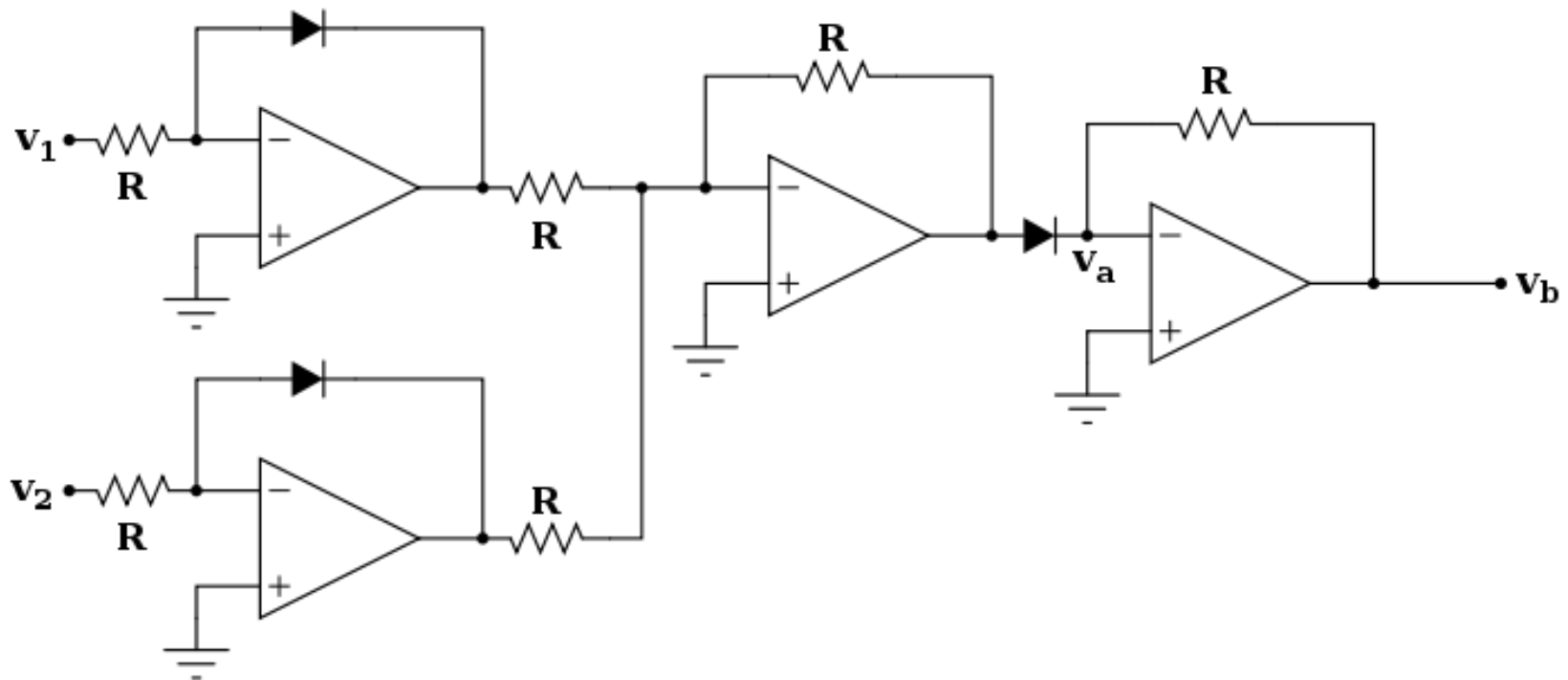


Signal multiplication

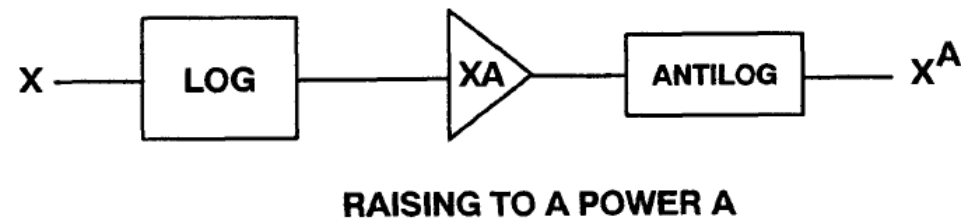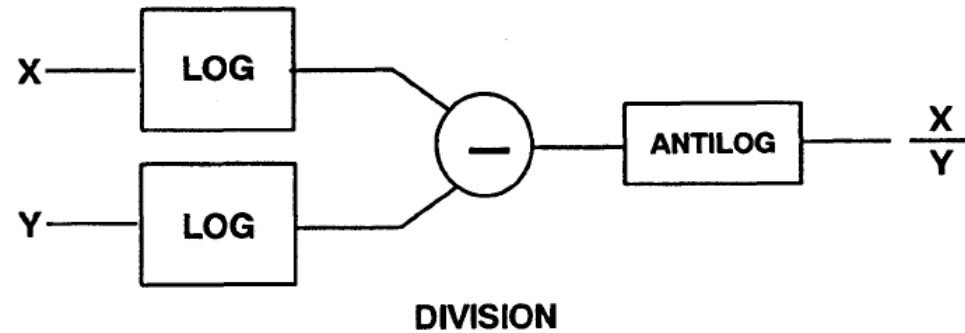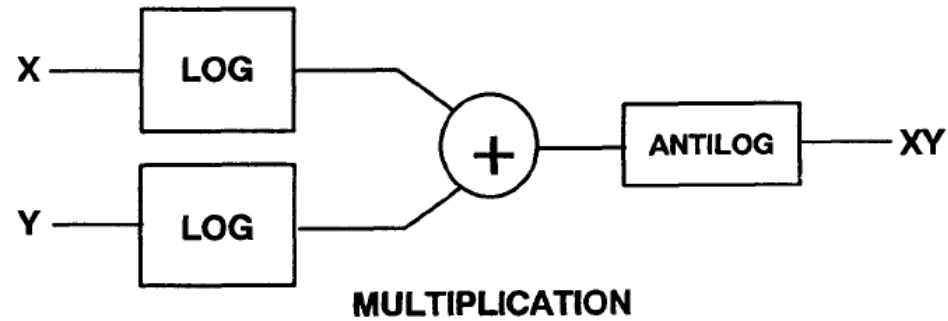

Low Pass Filter

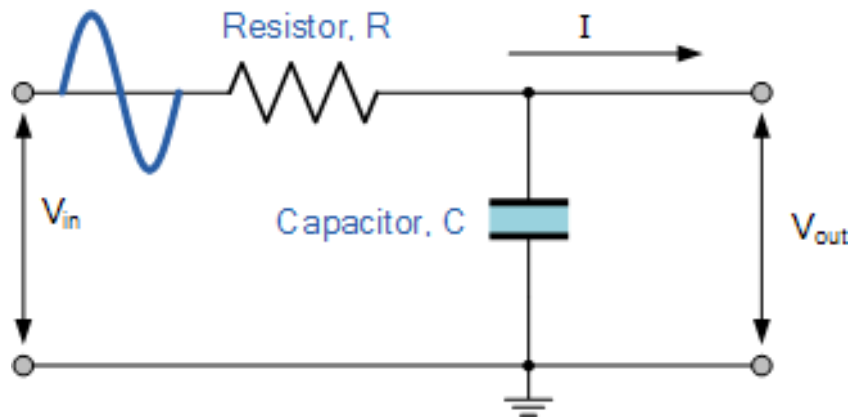


Passive Low Pass Filter

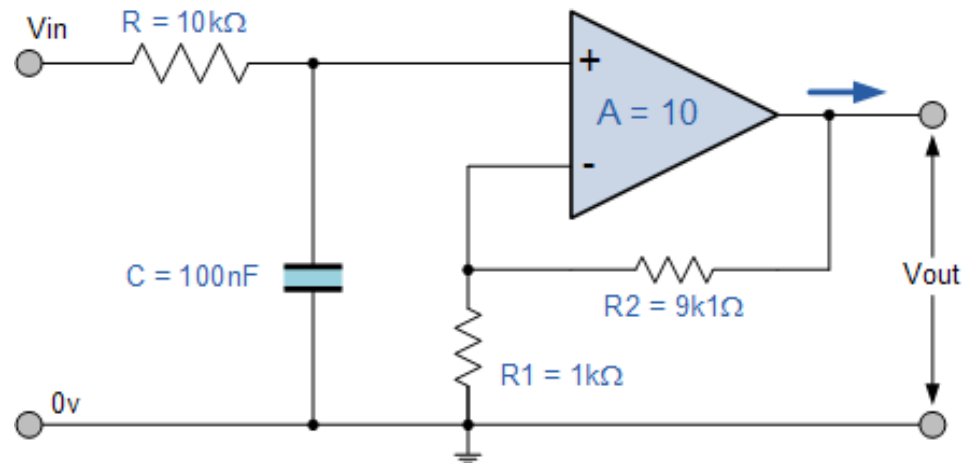


Active Low Pass Filter

High Pass Filter

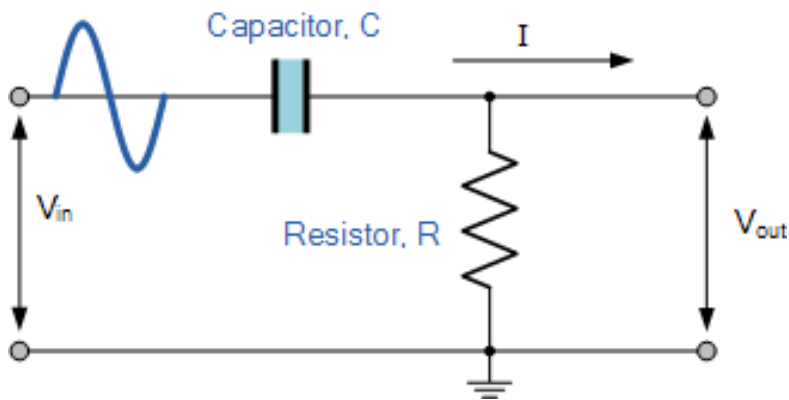

Passive High Pass Filter

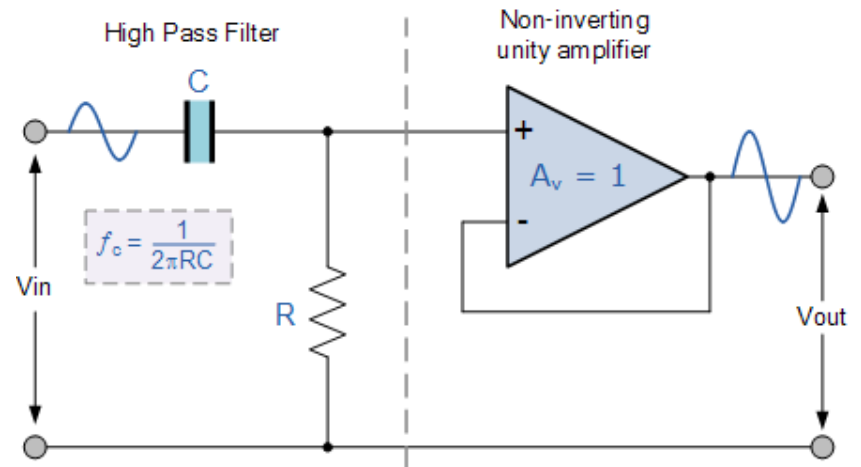

Active High Pass Filter