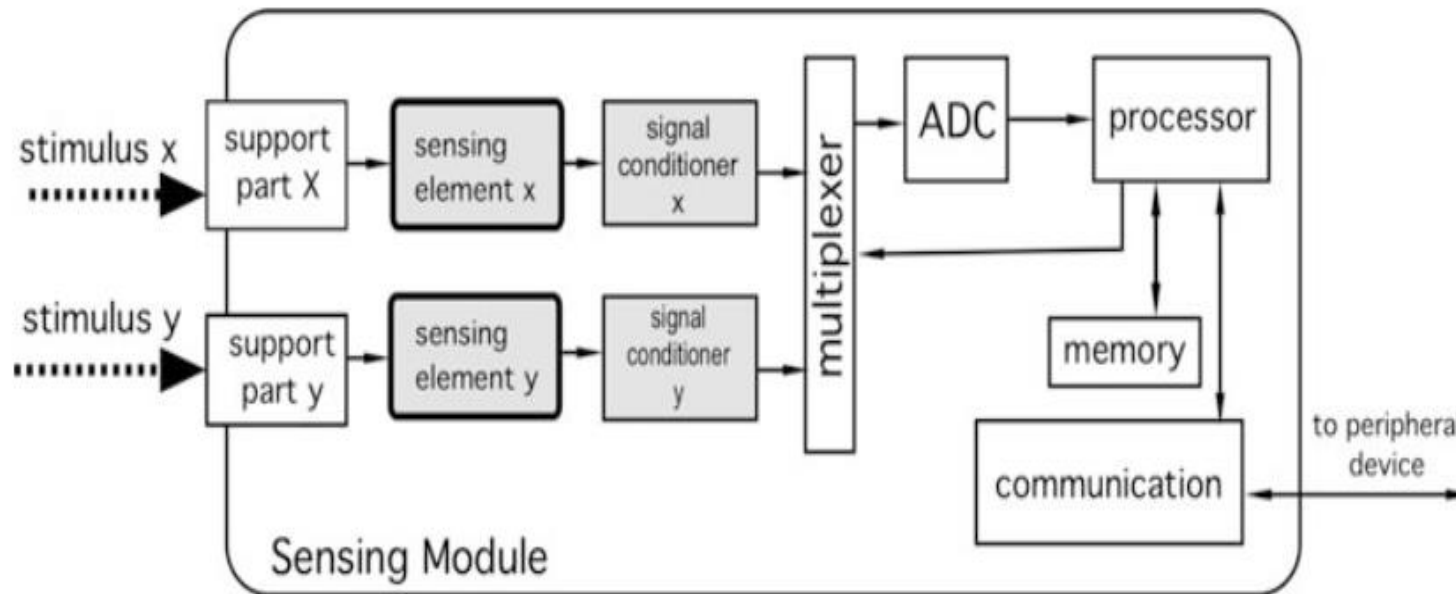


Interface Electronic Circuits



Signal Conditioner Circuit

Measurement systems block diagram



Circuit Input impedance

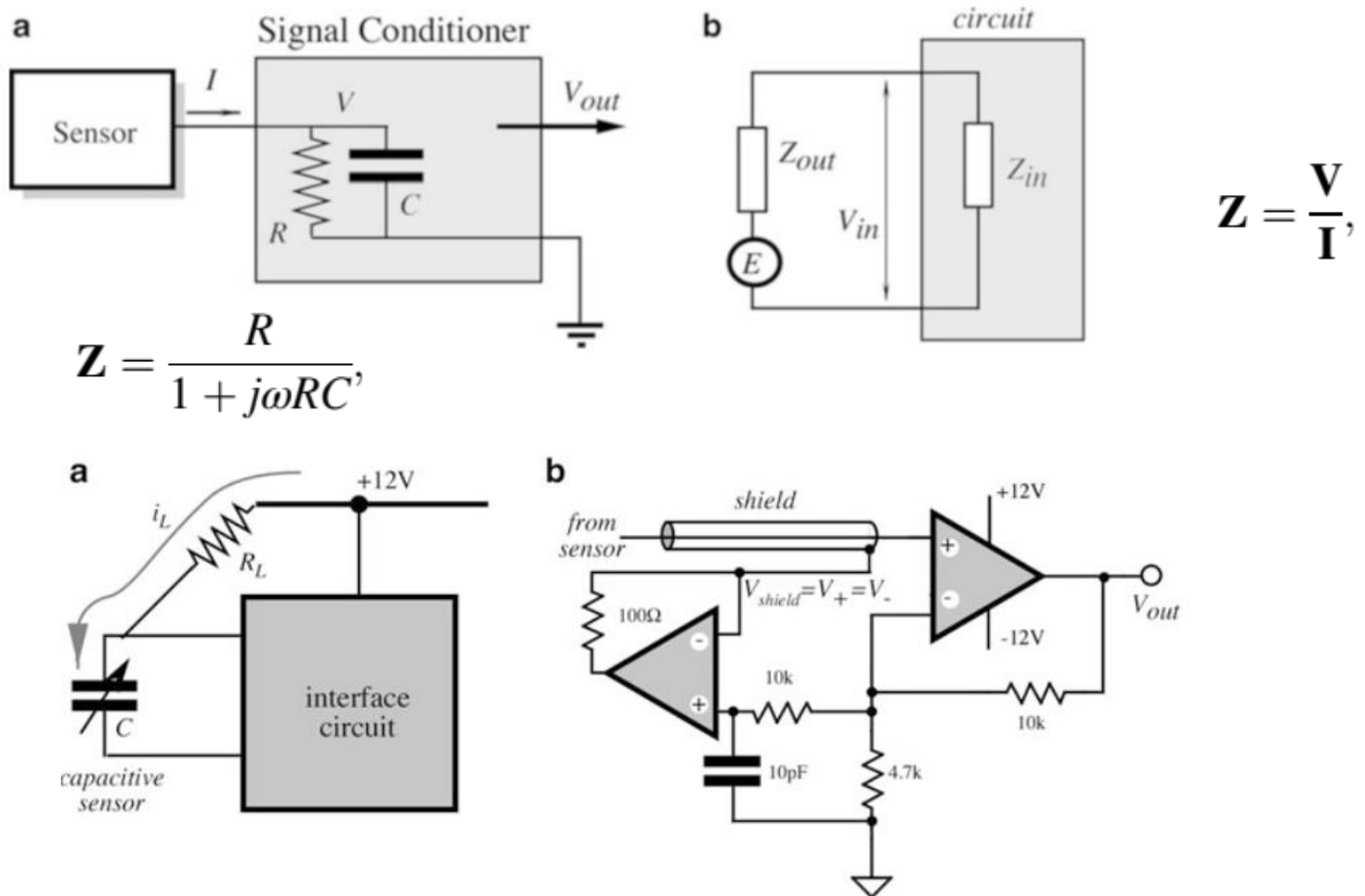


Fig. 6.4 Circuit board leakage affects input stage (a); driven shield of input stage (b)

Current to Voltage

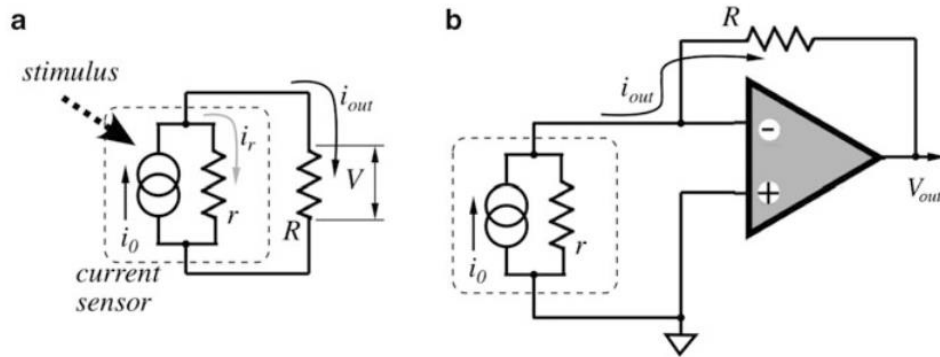


Fig. 6.7 Current-to-voltage converters


$$V_{out} = -iR$$



Shunt Resistor

$$G_{INA210} = 100 \cdot \frac{R_{INA210}}{R_{INA210} + R_{FILT}}$$


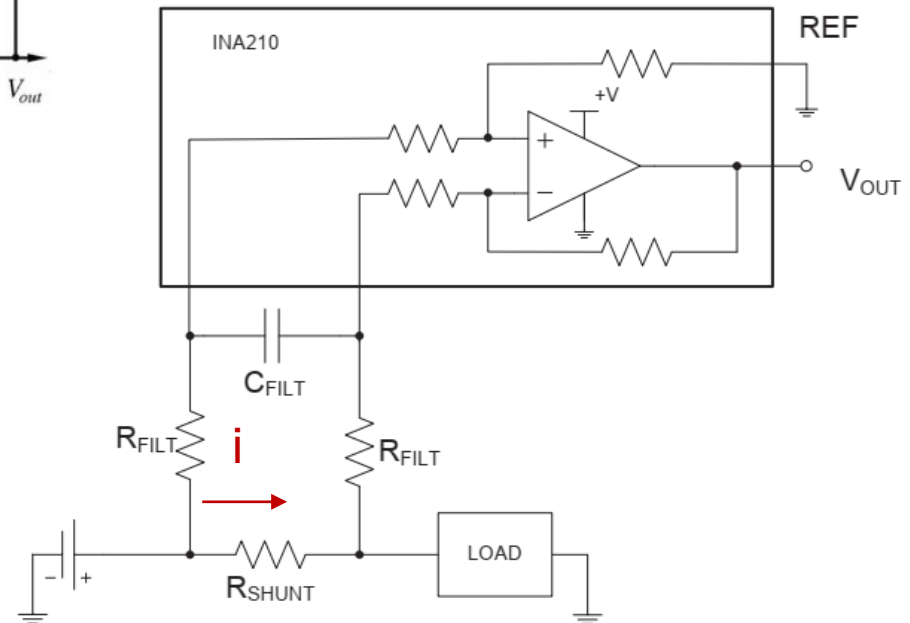
DOI: 10.1109/TSP.2011.6043770 · Source: DBLP



$$f_c = \frac{1}{2\pi \cdot (2R_{FILT}) \cdot C_{FILT}} \quad (3)$$

If we select a value 220 nF for C_{FILT} we get a cutoff frequency 7.7 kHz, which allows us to use a sampling frequency not lower than 15.4 kHz in accordance with the Nyquist theorem.

Current to Voltage

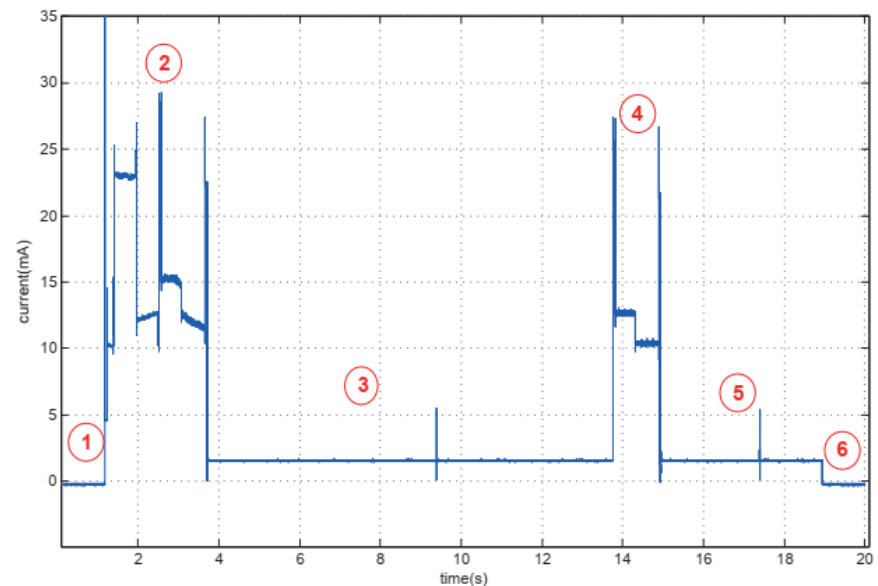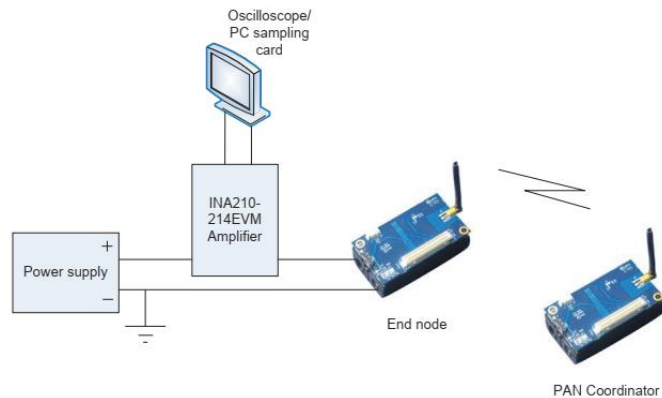

Phase 1: the node is turned off and the consumption is certainly 0.

Phase 2: Turning on the sensor node performs association and binding phase exchanging information with PAN Coordinator and initial packet transmission (phase 2).

Phase 3: node waits in a sleep mode (phase 3)

Phase 4: draining minimum of energy until periodic packet transmission takes place in phase 4.

Phase 5 represents waiting for next periodic packet transmission in the sleep mode, however, the end node is turned off (phase 6).

Light to Voltage

Light-to-voltage converters are required for converting output signals from photosensors to voltage

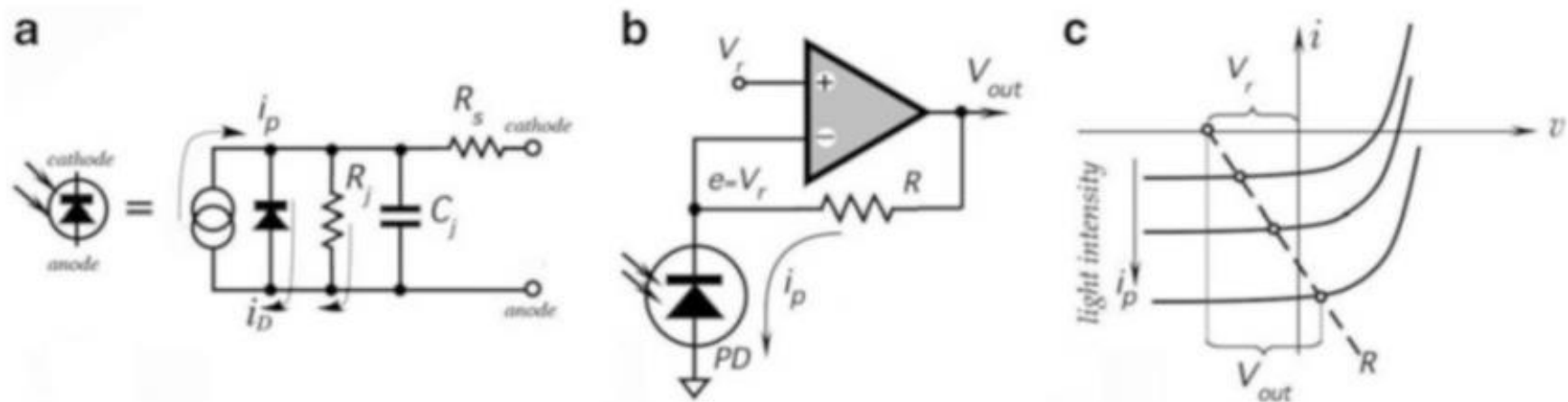


Fig. 6.8 Equivalent circuit of photodiode (a). Reverse-biased photodiode with current-to-voltage converter (b). Load diagram of circuit (c)

Light to Voltage

Photodiode Conditional circuit

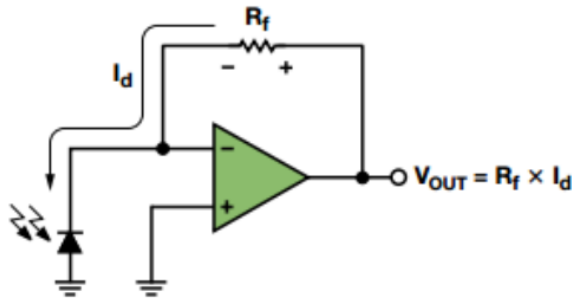


Figure 1. Simple Transimpedance Amplifier Circuit

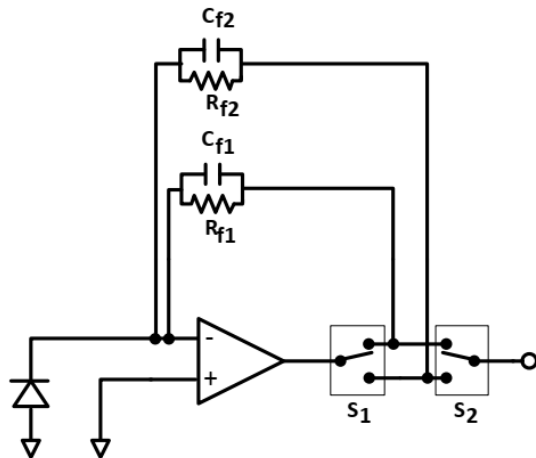


Figure 8. Using Two Sets of Switches Reduces Errors Due to Additional Resistance Inside the Loop

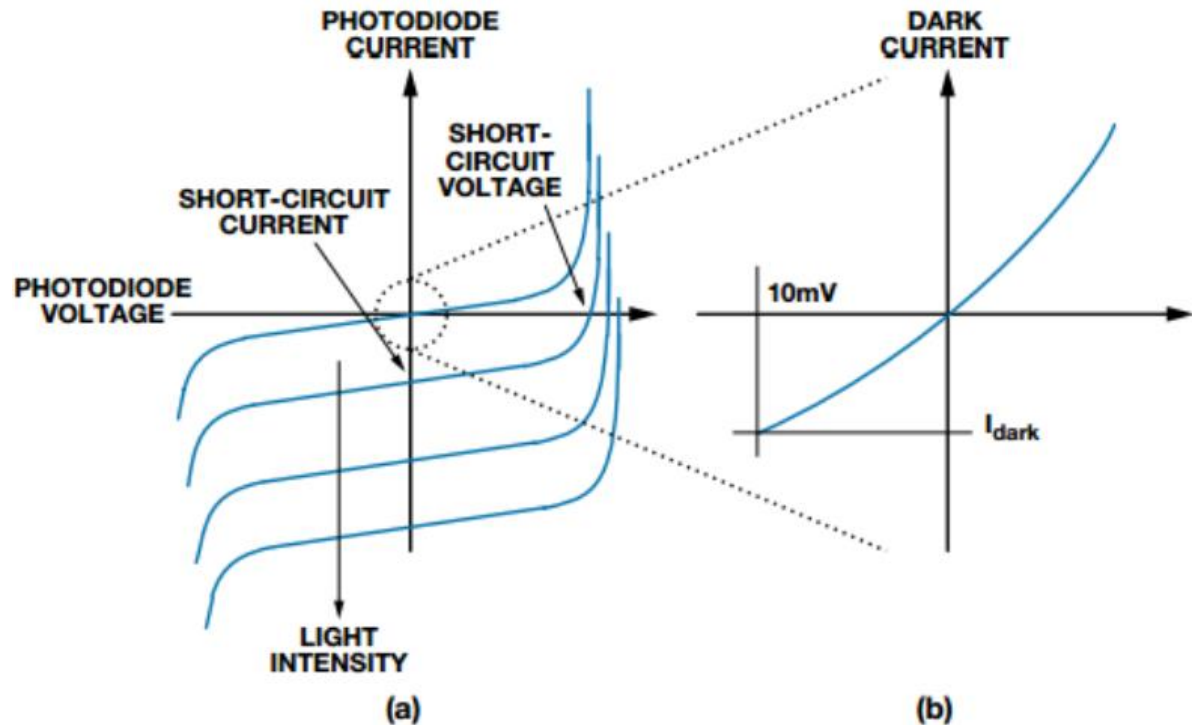


Figure 2. Typical Photodiode Transfer Function

Capacitance to Voltage Converter

Design of Capacitance to Voltage Converter for Capacitive Sensor Transducer

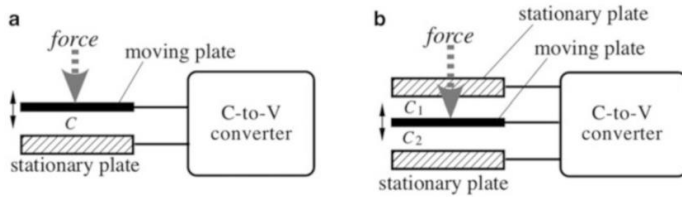


Fig. 6.10 Asymmetrical (a) and symmetrical (b) capacitive displacement sensor

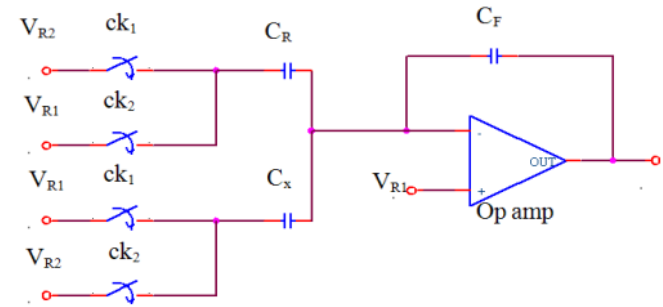


Fig. 1: Capacitance to Voltage Converter (CVC)

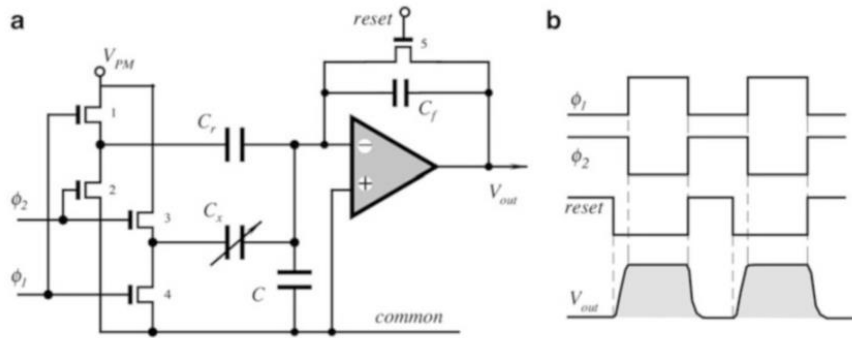


Fig. 6.11 Simplified schematic (a) and timing diagrams (b) of capacitance-to-voltage converter using switched-capacitors technique

$$V_o = \frac{C_x - C_R}{C_F} (V_{R2} - V_{R1}) \times \left(\frac{1}{1 + \frac{1}{A} \left(\frac{C_F + C_R + C_x}{C_F} \right)} \right) \quad (5)$$

$$= \frac{C_x - C_R}{C_F} (V_{R2} - V_{R1}) \times \left(1 - \frac{1}{A \left(\frac{C_F}{C_F + C_R + C} \right)} \right)$$

Capacitance to Voltage Converter

OPA: bandwidth gain is approximately 1.8 MHz.

The detection capacitance C_x is varied from 20- 1700 fF

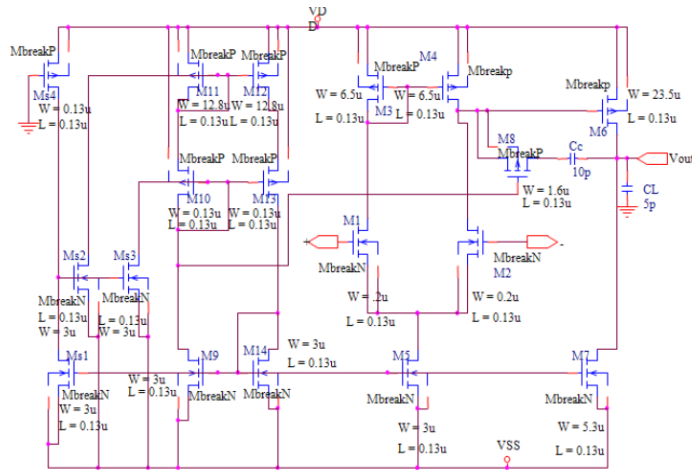


Fig. 2: Schematic for Op amp

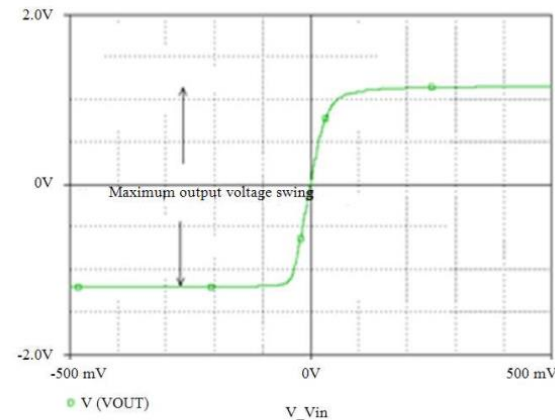
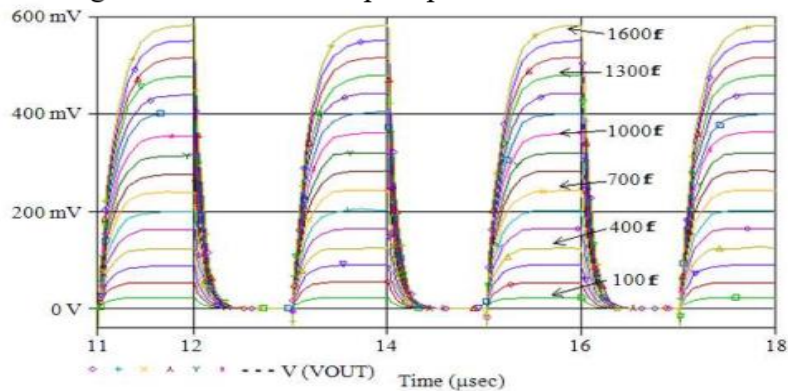


Fig. 3: Voltage transfer characteristics of the Op amp

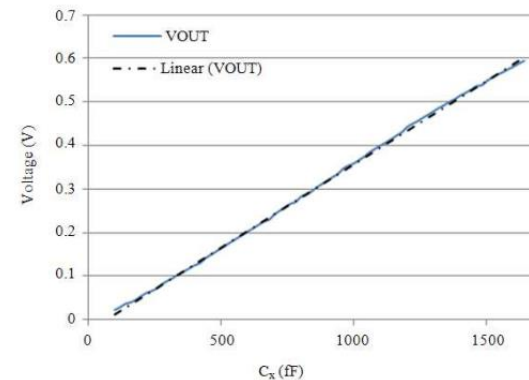


Fig. 6: Peak output voltage with the variation of C_x

Excitation Circuit

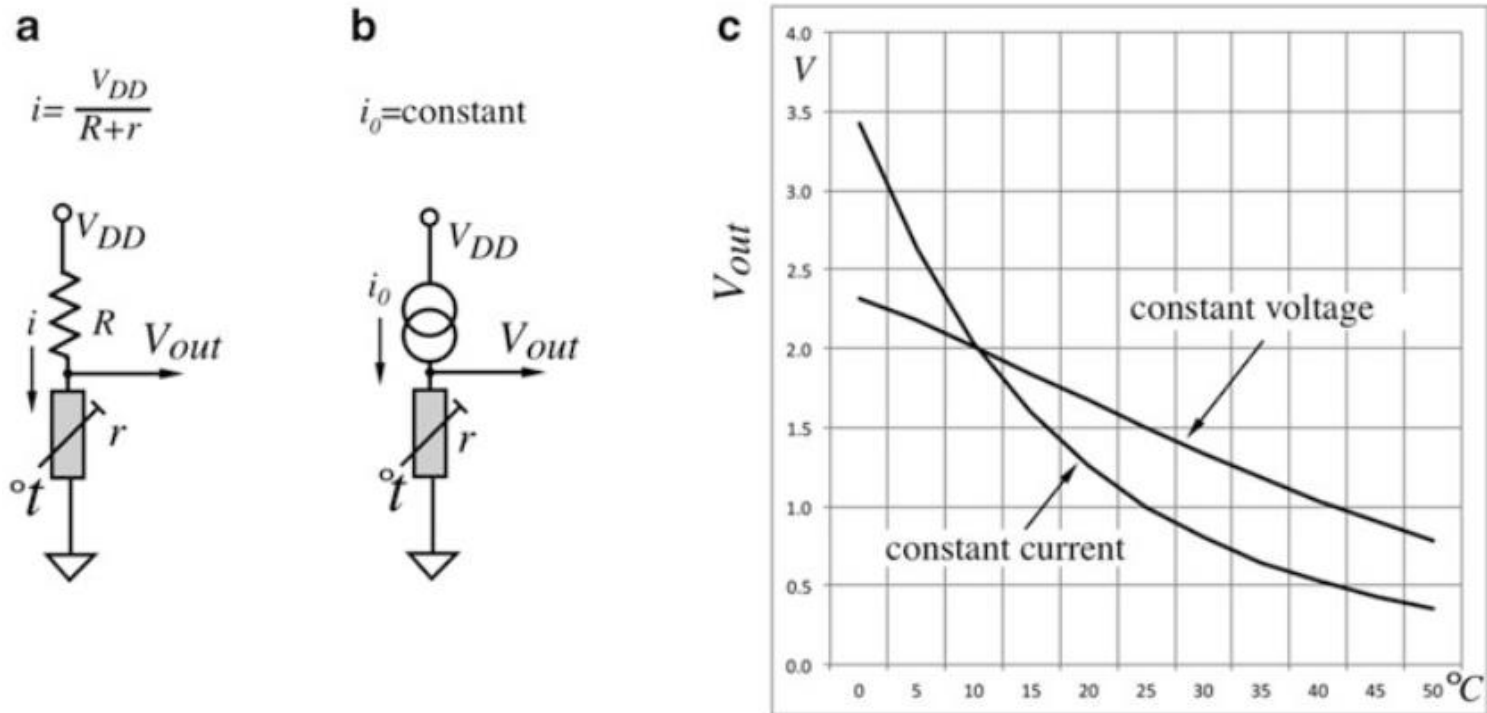


Fig. 6.20 Generating of excitation currents by a constant voltage source V_{DD} (a) and by constant current source i_0 (b); voltages across thermistor r at two different excitation currents as functions of temperature (c)

Excitation Circuit- Current Source

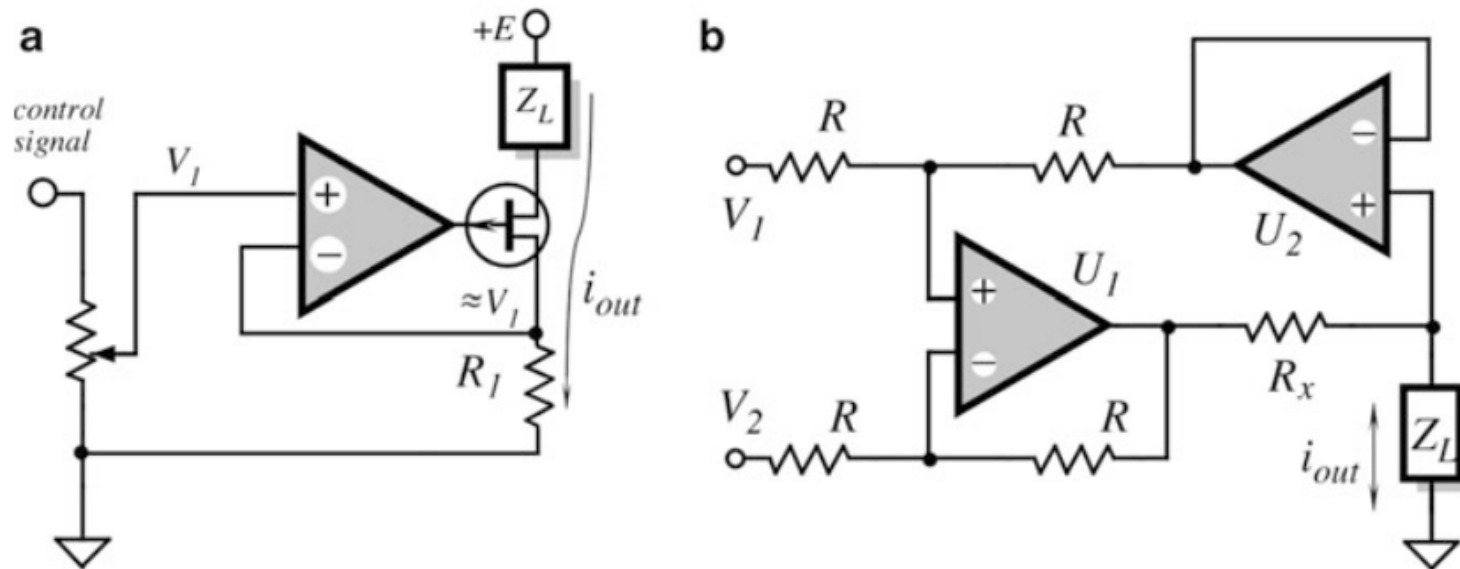



Fig. 6.21 Current sink with JFET transistor (a) and Howland current pump (b)

$$i_L = \frac{(V_1 - V_2)}{R_s}.$$

Wheatstone Bridge Circuit

□ Wheatstone Bridge

Fig. 6.16 General circuit of Wheatstone bridge (a) and half-bridge (b)

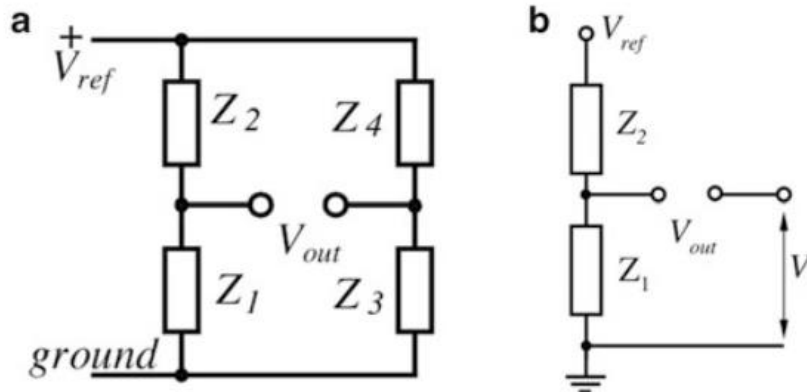

$$V_{out} = \left(\frac{Z_1}{Z_1 + Z_2} - \frac{Z_3}{Z_3 + Z_4} \right) V_{ref} = V_{ref} \left[\left(1 + \frac{Z_2}{Z_1} \right)^{-1} - \left(1 + \frac{Z_4}{Z_3} \right)^{-1} \right]$$

$$\frac{\partial V_{out}}{\partial Z_1} = \frac{Z_2}{(Z_1 + Z_2)^2} V_{ref}$$





$$\frac{\partial V_{out}}{\partial Z_2} = -\frac{Z_1}{(Z_1 + Z_2)^2} V_{ref}$$

$$\frac{\partial V_{out}}{\partial Z_3} = -\frac{Z_4}{(Z_3 + Z_4)^2} V_{ref}$$

$$\frac{\partial V_{out}}{\partial Z_4} = \frac{Z_3}{(Z_3 + Z_4)^2} V_{ref}$$

$$\text{If } (Z_1 = Z_2) \rightarrow \frac{\delta V_{out}}{V_{ref}} = \frac{\delta Z_1}{4Z_1}$$

Wheatstone Bridge Circuit

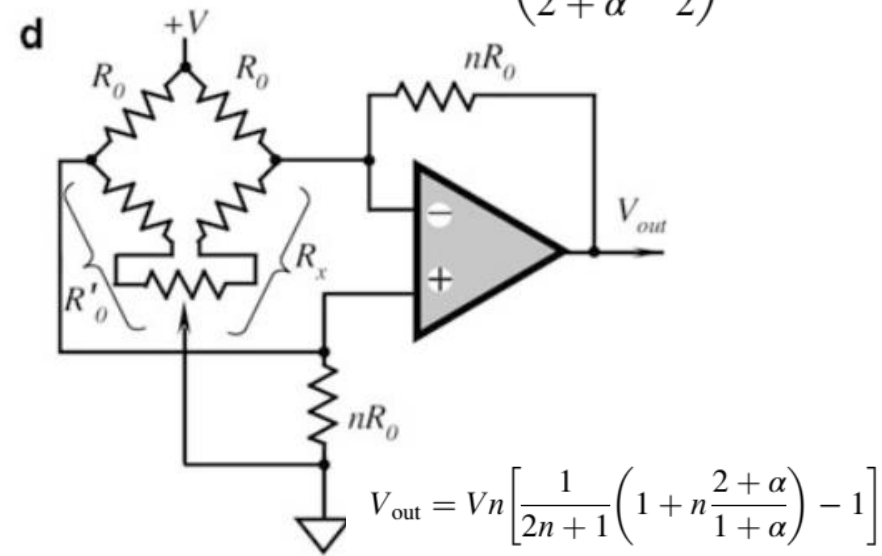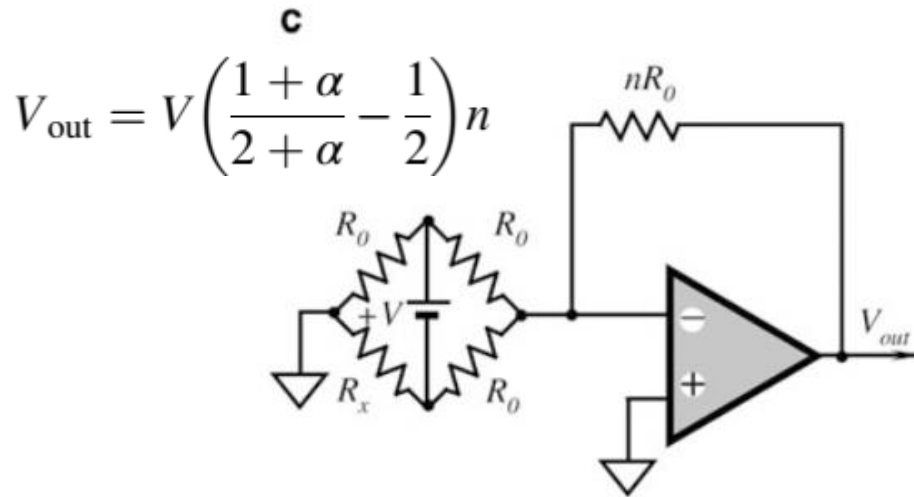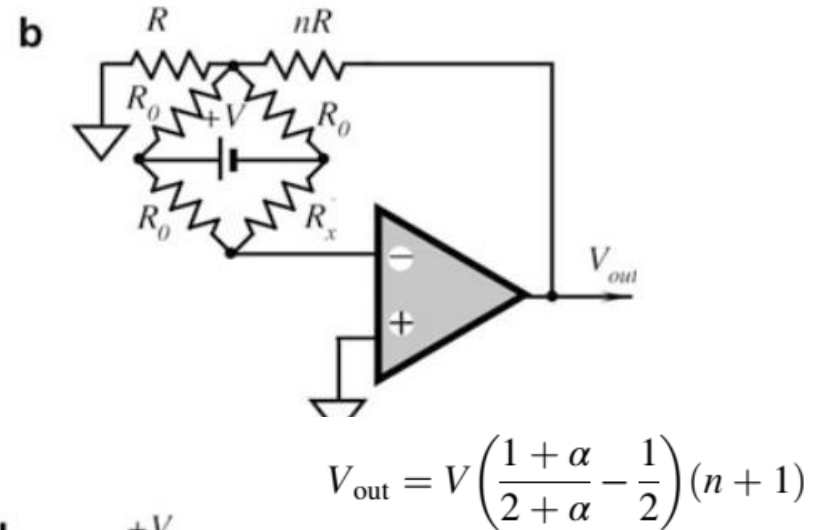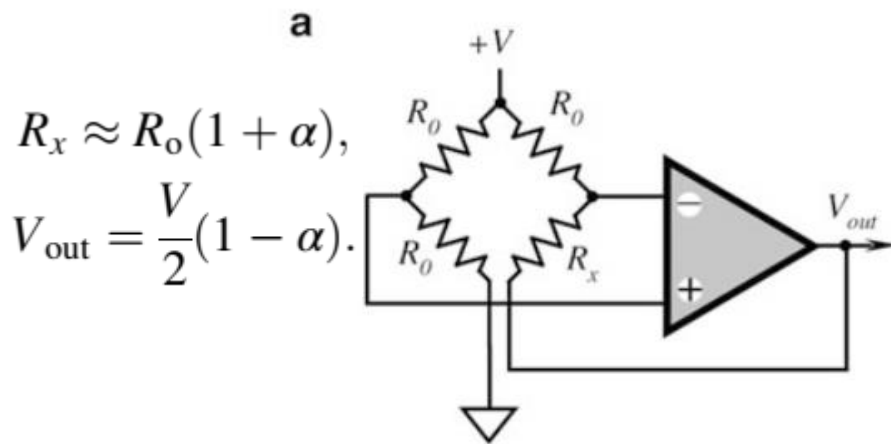

ADC Interface

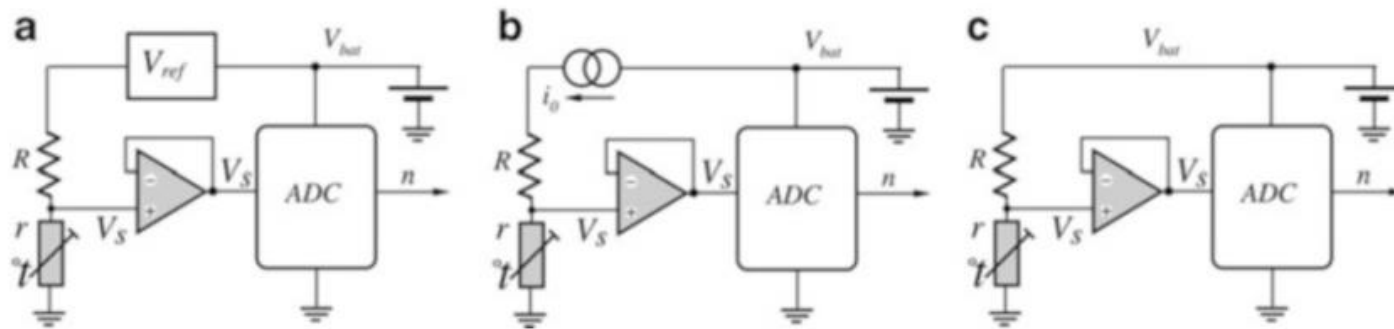


Fig. 6.33 Powering the sensor circuit with constant voltage (a), constant current (b), and ratiometric voltage (c)


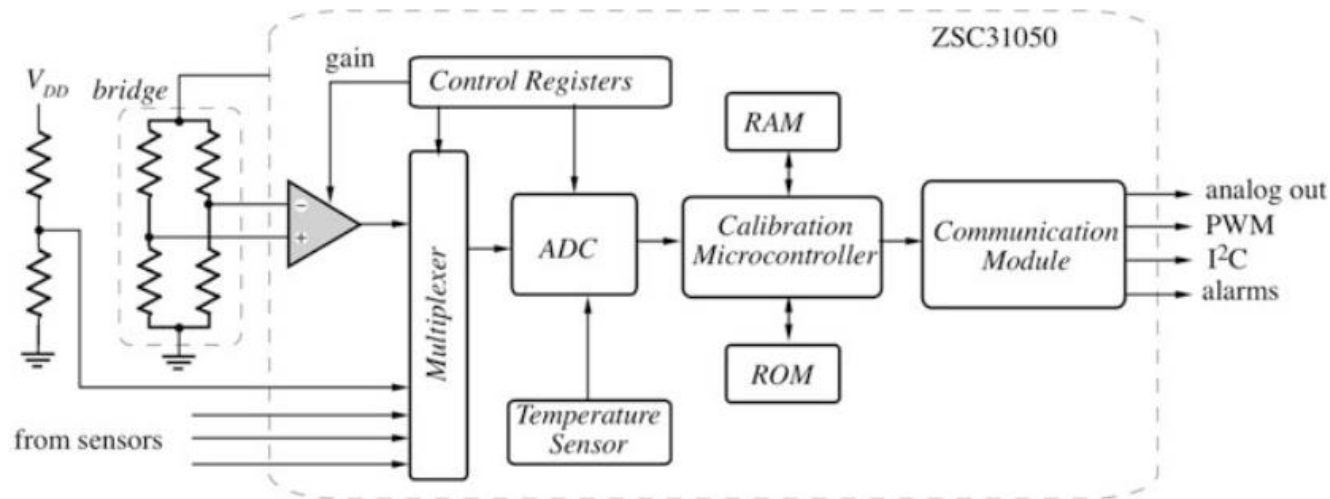


Fig. 6.34 Integrated ZMDI Signal Conditioner

ADC Interface

□ ADC input

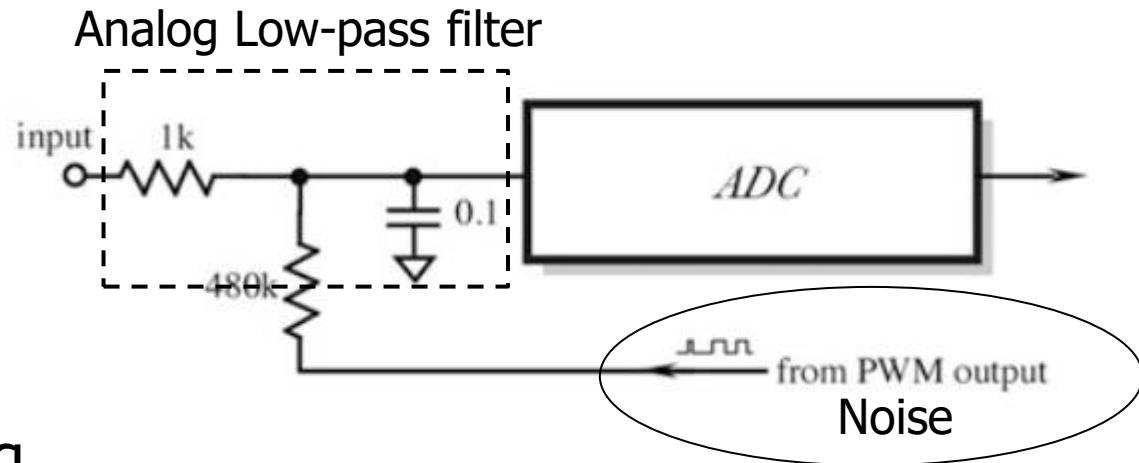

□ ADC Sampling

Digital Filter:

- Average Number of Samples per one point
- Design a digital Low-pass filter with code
- Kalman Filter


Noise in Sensor and Circuit

□ Inherent Noise

The movement of carriers are temperature related and noise power, in turn, is also temperature related. In a resistor, these thermal motions cause Johnson noise. The mean-square value of noise voltage (which is representative of noise power) can be calculated from:

$$\overline{e_n^2} = 4kTR\Delta f \quad [\text{V}^2/\text{Hz}]$$

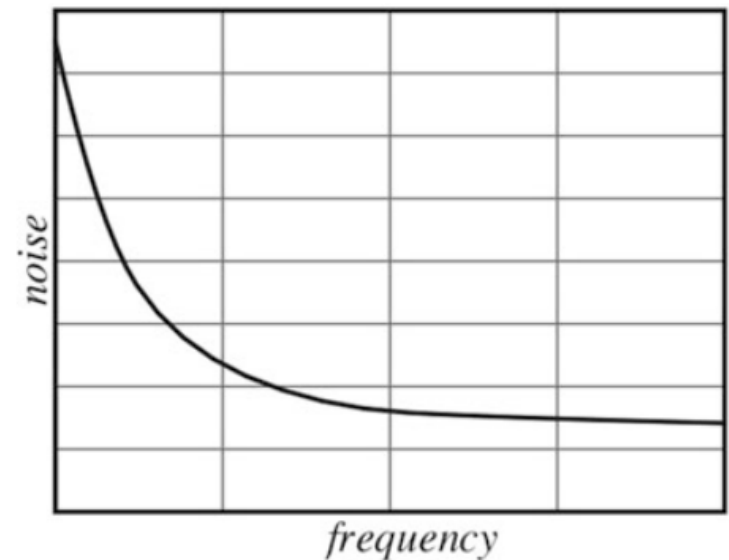
$$\downarrow$$
$$\overline{e_n} \approx 0.13\sqrt{R \cdot \Delta f} \quad \text{in nV.}$$



Spectral distribution of 1/f “pink” noise

Noise in Sensor and Circuit

□ Transmitted Noise

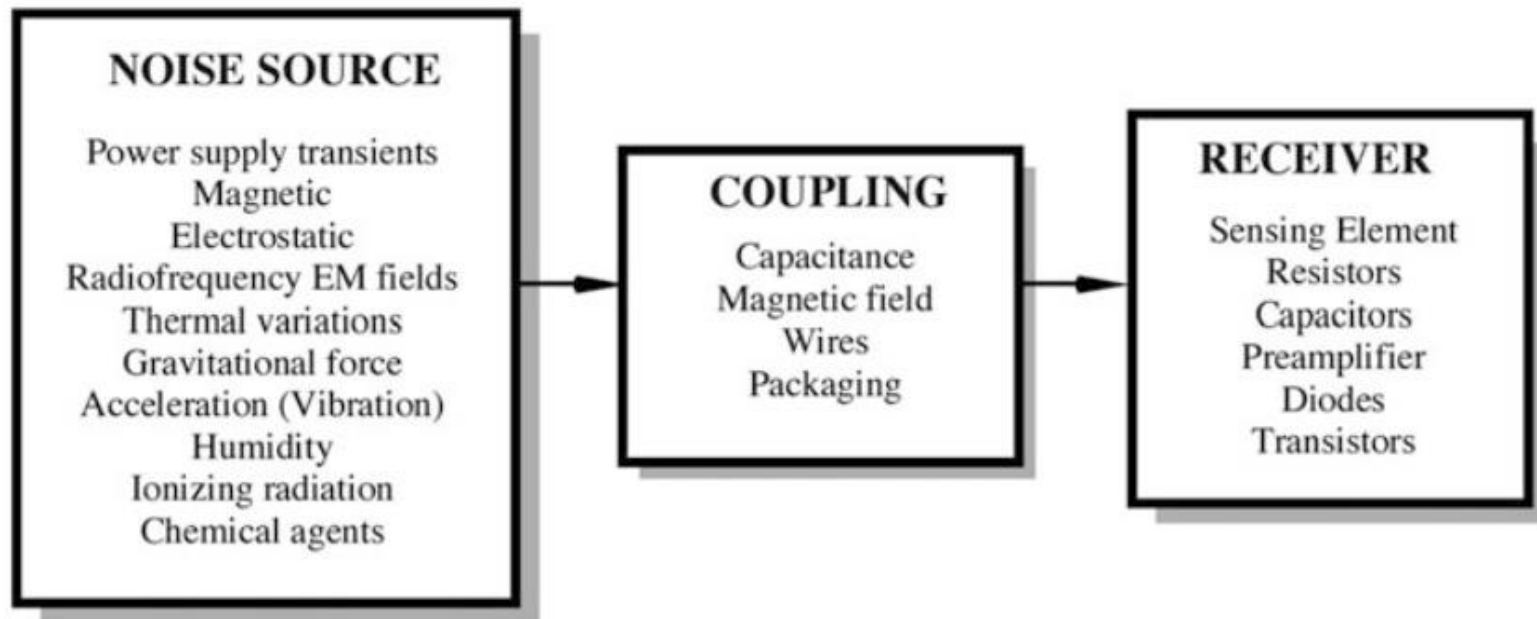


Sources and coupling of transmitted noise


Noise in Sensor and Circuit

□ Additive Noise

$$V_{out} = V_s + e_n.$$

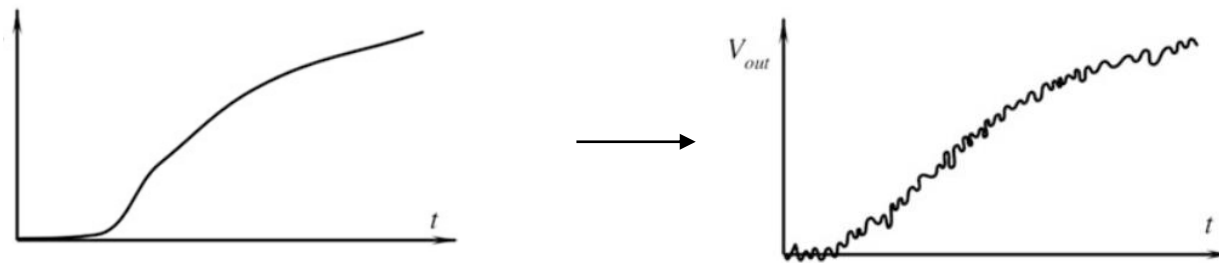

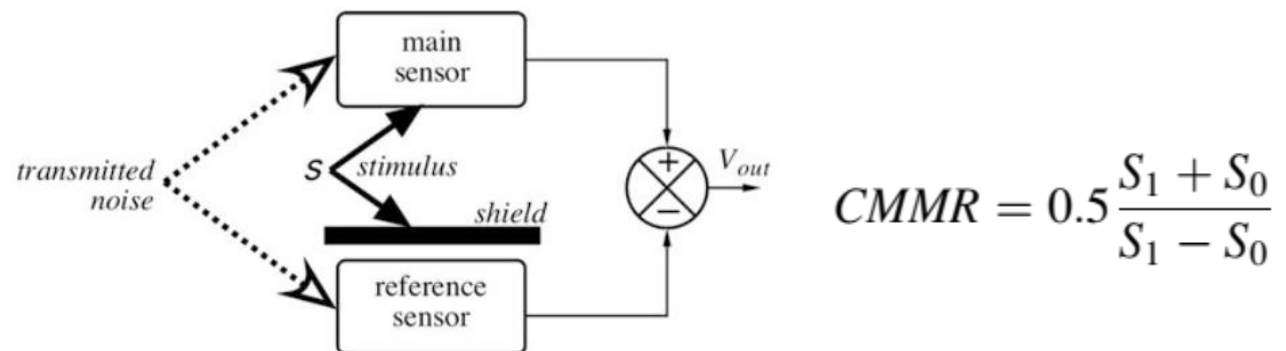□ Shield prevents stimulus s from reaching reference sensor



Noise in Sensor and Circuit

□ Improve noise-Electrical Shield



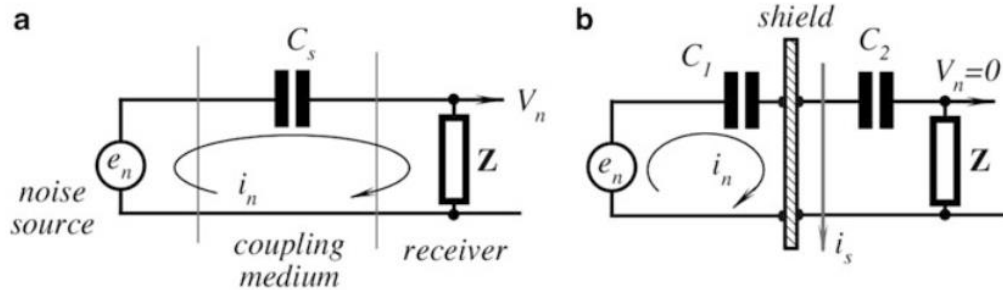


Fig. 6.43 Capacitive coupling (a) and electric shield (b)

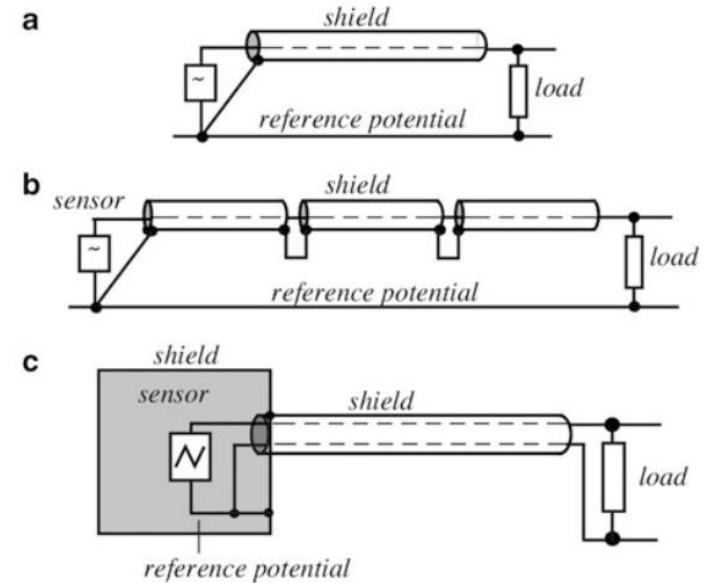

□ Bypass Capacitors

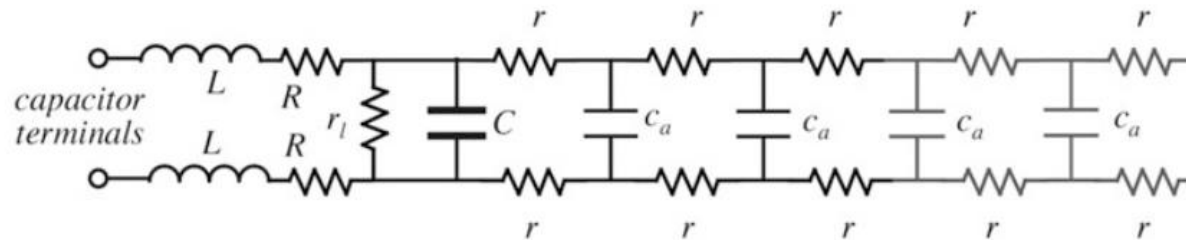

Noise in Sensor and Circuit

Seebeck Noise

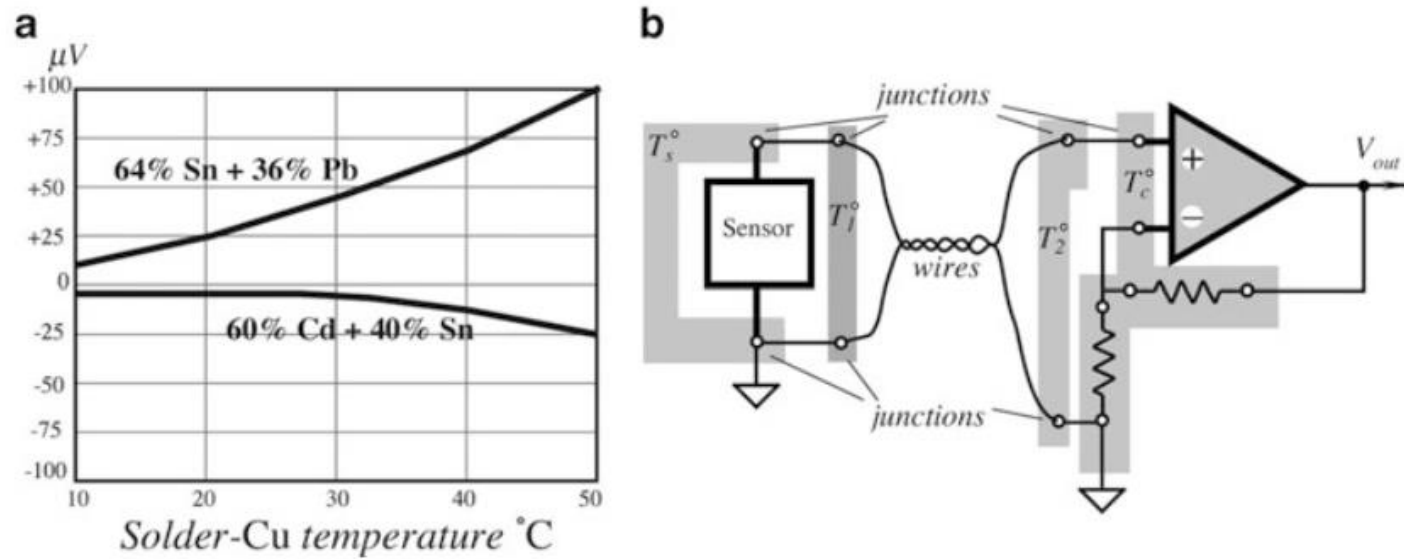


Fig. 6.51 Seebeck *e.m.f.* developed by solder-copper joints (a) (adapted from [14]); maintaining joints at the same temperature reduces Seebeck noise (b)